


# 4. Combinational Logic

6.004x Computation Structures  
Part 1 – Digital Circuits

Copyright © 2015 MIT EECS
 
# Functional Specifications

There are many ways of specifying the function of a combinational device, for example:



Concise alternatives:

- *truth tables* are a concise description of the combinational system's function.
- *Boolean expressions* form an algebra whose operations are AND (multiplication), OR (addition), and inversion (overbar).

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Y = \bar{C} \cdot \bar{B} \cdot A + \bar{C}BA + C\bar{B}\bar{A} + CBA$$

Any combinational (Boolean) function can be specified as a truth table or an equivalent sum-of-products Boolean expression!

# Here's a Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

1. Write out our functional spec as a truth table
2. Write down a Boolean expression with terms covering each '1' in the output:


$$Y = \bar{C}\bar{B}A + \bar{C}BA + C\bar{B}\bar{A} + CBA$$


3. We'll show how to build a circuit using this equation in the next two slides.

This approach will always give us Boolean expressions in a particular form: SUM-OF-PRODUCTS


# Sum-of-products Building Blocks

INVERTER:

 


<b>A</b>	<b>Z</b>
<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>

AND:

 

<b>A</b>	<b>B</b>	<b>Z</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>

OR:

 


<b>A</b>	<b>B</b>	<b>Z</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>

# Straightforward Synthesis

We can implement  
SUM-OF-PRODUCTS  
with just three levels of  
logic:


1. Inverters
2. ANDs
3. OR

 

*-it's systematic!  
-it works!  
-it's easy!  
-are we done yet???*


Propagation delay --  
No more than 3 gate delays?\*

 \*assuming gates with an arbitrary number of inputs,  
which, as we'll see, isn't a good assumption!



 
# ANDs and ORs with > 2 Inputs



Replace 2-input AND gates with 2-input OR gates to create large fan-in OR gates.



 Chain: Propagation delay increases linearly with number of inputs




*Which one should I use?*

  

Tree: Propagation delay increases logarithmically with number of inputs


# More Building Blocks

NAND (not AND)

 

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0


NOR (not OR)

 

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

In a CMOS gate, rising inputs lead to falling outputs and vice-versa, so CMOS gates are naturally inverting. Want to use NANDs and NORs in CMOS designs... But **NAND and NOR operations are not associative**, so wide NAND and NOR gate can't use a chain or tree strategy. Stay tuned for more on this!

XOR (exclusive OR)

 


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

**XOR is very useful when implementing parity and arithmetic logic. Also used as a "programmable inverter": if A=0, Z=B; if A=1, Z=~B**

**Wide fan-in XORs can be created with chains or trees of 2-input XORs.**

# Universal Building Blocks

NANDs and NORs are universal:

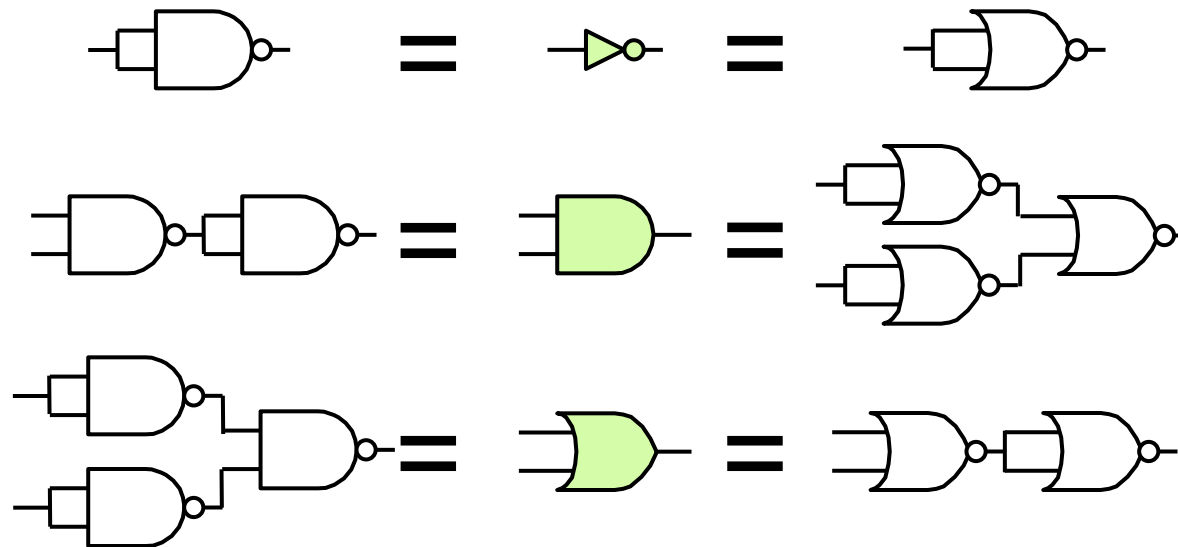


Any logic function can be implemented using only NANDs (or, equivalently, NORs). Good news for CMOS technologies!




# CMOS ♥ Inverting Logic

See “The Standard Cell Library” handout in *Updates & Handouts*

 


AND4:
 
$$t_{PD} = 160 \text{ ps, size} = 20 \mu^2$$



NAND4 + INV:
 
$$t_{PD} = 90 \text{ ps, size} = 27 \mu^2$$




Demorgan's  $\overline{A \cdot B} = \overline{A + B}$   
Laws:  $\overline{A + B} = \overline{A} \cdot \overline{B}$

2\*NAND2 + NOR2:



$$t_{PD} = 80 \text{ ps, size} = 30 \mu^2$$
 
# Wide NANDs and NORs

Most logic libraries include 2-, 3- and 4-input devices:




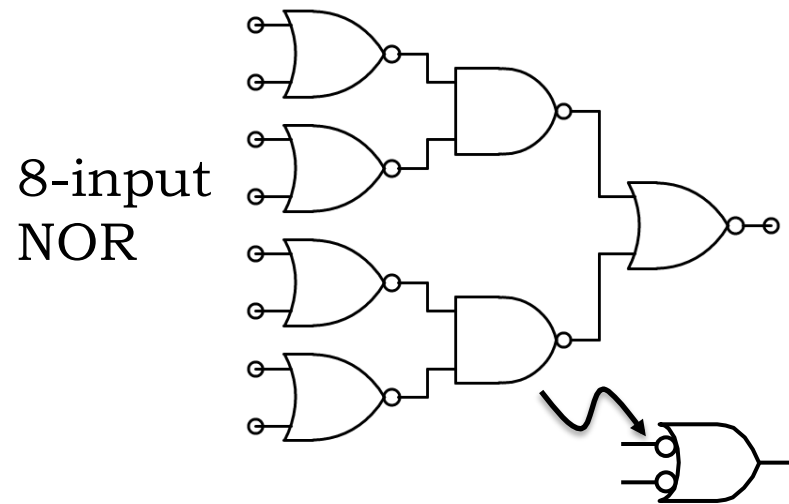 But for a large number of inputs, the series connections of too many MOSFETs can lead to very large effective R. Design note: use trees of smaller devices...




# CMOS Sum-of-products Implementation


NAND-NAND

 
 
$$\overline{\overline{A}\overline{B}} = \overline{\overline{A+B}}$$




“Pushing Bubbles”


 


$$\overline{A}\overline{C} + AB + BC$$

NOR-NOR

 
  
$$\overline{\overline{\overline{A}\overline{B}}} = \overline{\overline{A+B}}$$



$$\overline{A}\overline{C} + AB + BC$$

*You might think all these extra inverters would make this structure less attractive. However, quite the opposite is true.*



# Logic Simplification

Can we implement the same function with fewer gates? Before trying we'll add a few more tricks in our bag.

BOOLEAN ALGEBRA:

OR rules:  $a + 1 = 1$ ,  $a + 0 = a$ ,  $a + a = a$

AND rules:  $a1 = a$ ,  $a0 = 0$ ,  $aa = a$

Commutative:  $a + b = b + a$ ,  $ab = ba$

Associative:  $(a + b) + c = a + (b + c)$ ,  $(ab)c = a(bc)$

Distributive:  $a(b+c) = ab + ac$ ,  $a + bc = (a+b)(a+c)$

Complements:  $a + \bar{a} = 1$ ,  $a\bar{a} = 0$

Absorption:  $a + ab = a$ ,  $a + \bar{a}b = a + b$      $a(a + b) = a$ ,  $a(\bar{a} + b) = ab$

Reduction:  $ab + \bar{a}b = b$ ,  $(a + b)(\bar{a} + b) = b$

DeMorgan's Law:  $\bar{a} + \bar{b} = \overline{ab}$ ,  $\overline{\bar{a}\bar{b}} = a + b$

# Boolean Minimization

Let's (again!) simplify

$$Y = \overline{C}\overline{B}A + C\overline{B}\overline{A} + CBA + \overline{C}BA$$

Using the identity

$$\alpha A + \alpha \overline{A} = \alpha(A + \overline{A}) = \alpha \cdot 1 = \alpha$$


For any expression  $\alpha$  and variable A:

$$Y = \overline{C}\overline{B}A + C\overline{B}\overline{A} + CBA + \overline{C}BA$$


$$Y = \overline{C}\overline{B}A + CB + \overline{C}BA$$

$$Y = \overline{C}A + CB$$

 *Can't he come up  
with a new example???*



 *Hey... I could write  
a program to do  
that*



# Truth Tables with “Don’t Cares”

One way to reveal the opportunities for a more compact implementation is to rewrite the truth table using “don’t cares” (– or X) to indicate when the value of a particular input is irrelevant in determining the value of the output.

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

C	B	A	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1
X	0	0	0
X	1	1	1

→  $\bar{C}A$

→  $CB$

→  $BA$

Note: Some input combinations (e.g., 000) are matched by more than one row in the “don’t care” table. It would be a bug if all the matching rows didn’t specify the same output value!


# The Case for a Non-minimal SOP

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$\bar{C}A$


$CB$

$BA$

 


$$Y = \bar{C}A + CB$$

 
NOTE: The steady state behavior of these circuits is identical. They differ in their transient behavior.



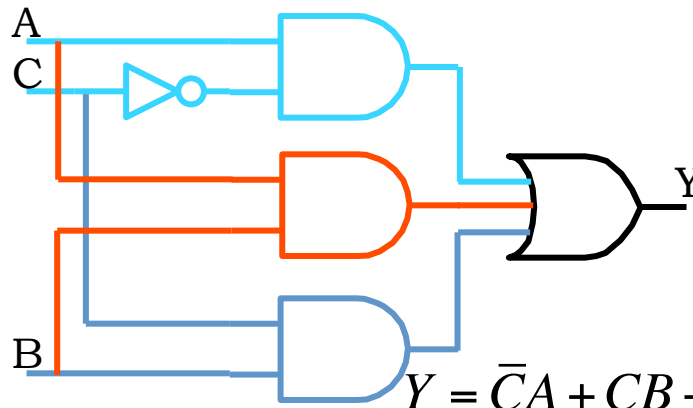That's what we call a "glitch" or "hazard"



$$Y = \bar{C}A + CB + AB$$

 

Now it's LENIENT!

# Karnaugh Maps: A Geometric Approach

K-Map: a truth table arranged so that terms which differ by exactly one variable are adjacent to one another so we can see potential reductions easily.

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Here's the layout of a 3-variable K-map filled in with the values from our truth table:

C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0



*Why did he shade that row Gray?*

 It's cyclic. The left edge is adjacent to the right edge. (It's really just a flattened out cube).





# Extending K-maps to 4-variable Tables

4-variable K-map  $F(A,B,C,D)$ :

$\backslash AB$ $CD \backslash$	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

Again it's cyclic. The left edge is adjacent to the right edge, and the top is adjacent to the bottom.

For functions of 5 or 6 variables, we'd need to use the 3<sup>rd</sup> dimension to build a 4x4x4 K-map. But then we're out of dimensions...

# Finding Implicants

An implicant

- is a rectangular region of the K-map where the function has the value 1 (i.e., a region that will need to be described by one or more product terms in the sum-of-products)
- has a width and length that must be a power of 2: 1, 2, 4
- can overlap other implicants
- is a prime implicant if it is not completely contained in any other implicant.

C\AB	00	01	11	10
0	0	0	1	1
1	1	0	0	0

$\overline{A}\overline{C}$  (pointing to the top-right 2x2 region of 1s)  
 $\overline{A}\overline{B}C$  (pointing to the bottom-left 1)

C\AB	00	01	11	10
0	1	0	0	1
1	1	1	0	1

$\overline{A}C$  (pointing to the bottom-left 2x2 region of 1s)  
 $\overline{B}$  (pointing to the rightmost column of 1s)

- can be uniquely identified by a single product term. The larger the implicant, the smaller the product term.

# Finding Prime Implicants

We want to find all the prime implicants. The right strategy is a greedy one.

- Find the uncircled prime implicant with the greatest area
  - Order:  $4 \times 4 \Rightarrow 2 \times 4$  or  $4 \times 2 \Rightarrow 4 \times 1$  or  $1 \times 4$  or  $2 \times 2 \Rightarrow 2 \times 1$  or  $1 \times 2 \Rightarrow 1 \times 1$
  - Overlap is okay
- Circle it
- Repeat until all prime implicants are circled

$\backslash AB$ CD\ 00	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

# Write Down Equations

Picking just enough prime implicants to cover all the 1's in the KMap, combine equations to form minimal sum-of-products.

C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = A\bar{C} + BC$$

*We're done!*



\AB CD\	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

$$Y = D + B\bar{C} + A\bar{C} + \bar{B}C$$

*Minimal SOP is not necessarily unique!*




\AB CD\	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

$$Y = D + B\bar{C} + A\bar{C} + \bar{B}C$$
 
# Prime Implicants, Glitches & Leniency


This circuit produces a glitch on Y when A=1, B=1, C: 1→0




C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0



 To make the circuit lenient, include product terms for ALL prime implicants.



# We've Been Designing a Mux

 


2-input Multiplexer


Truth Table

S	D <sub>1</sub>	D <sub>0</sub>	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 MUXes can be generalized to  $2^k$  data inputs and  $k$  select inputs ...




 ... and implemented as a tree of smaller MUXes:



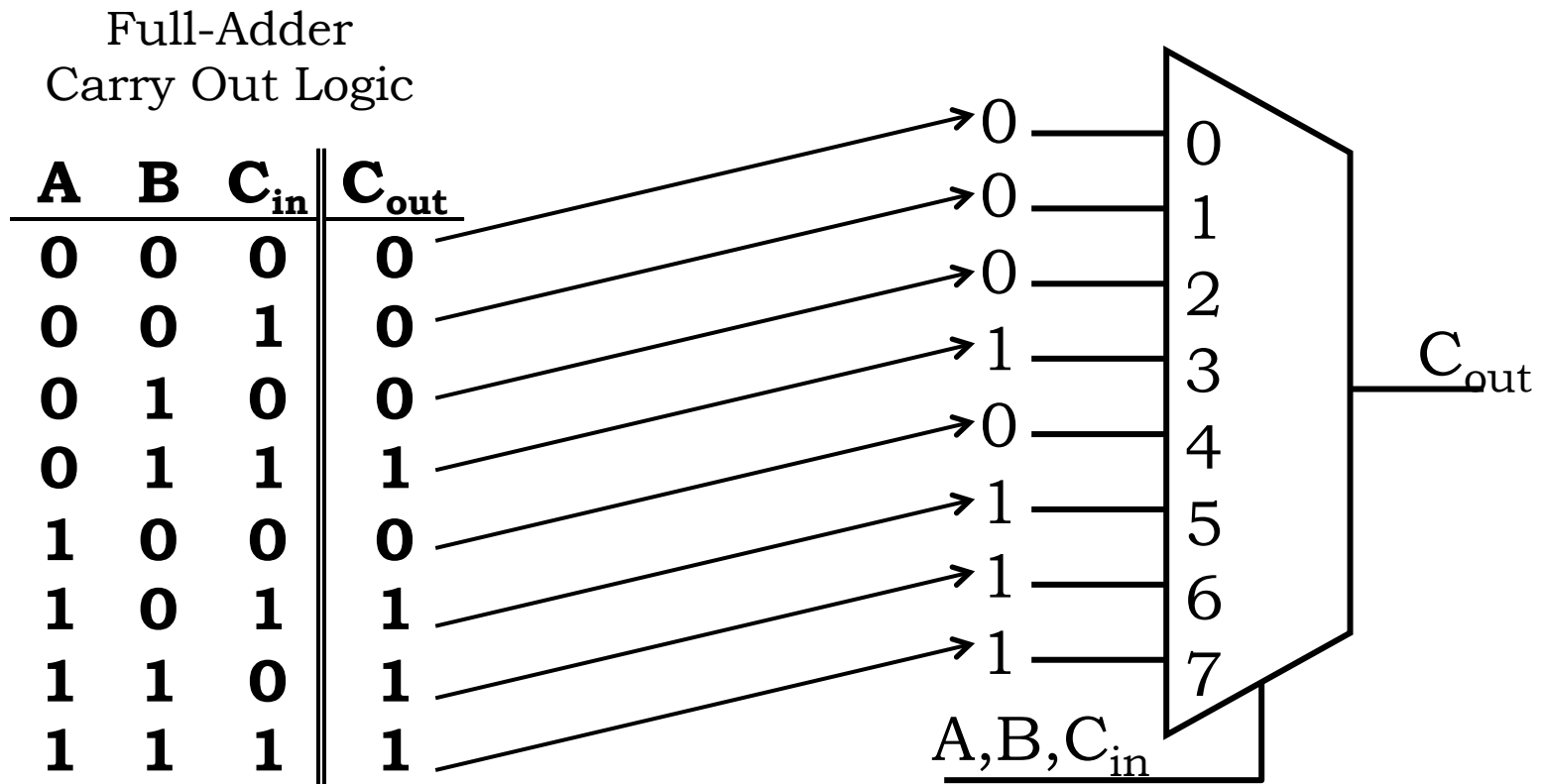
# Systematic Implementation Strategies

Consider implementing some arbitrary Boolean function,  $F(A,B,C)$  ... using a MULTIPLEXER as the only circuit element:



# Synthesis By Table Lookup

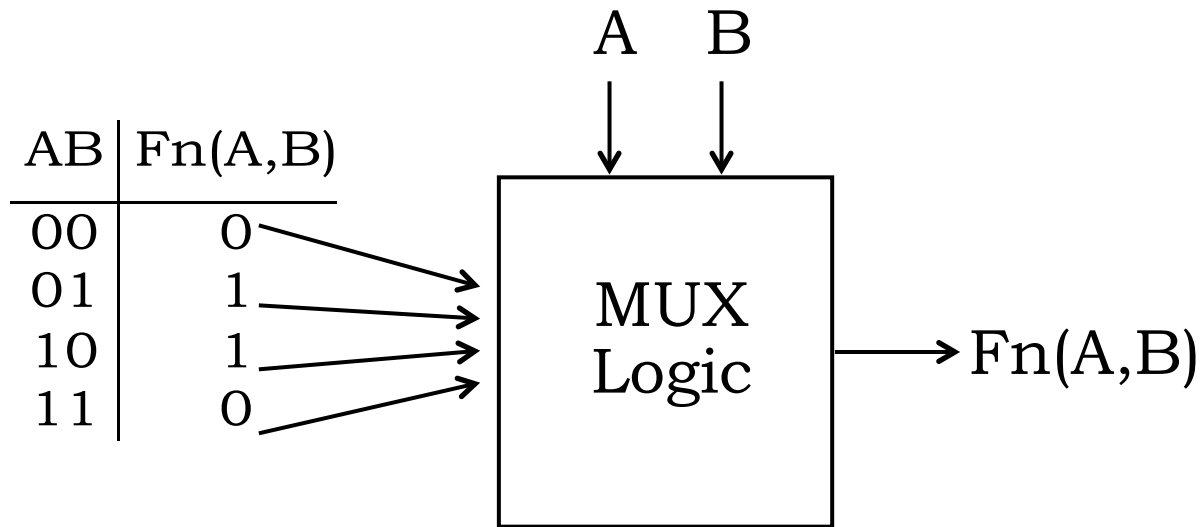

Generalizing:


In theory, we can build any 1-output combinational logic block with multiplexers.

For an N-input function we need a  $2^N$  input mux.

Is this practical for BIG truth tables?  
How about 10-input function? 20-input?


Muxes are universal!

 In future technologies muxes might be the “natural gate”.





# A New Combinational Device

 


DECODER:

- k SELECT inputs,
- $N = 2^k$  DATA OUTPUTS.

Select inputs choose one of the  $D_i$  to assert HIGH, all others will be LOW.

 *Have I mentioned that HIGH is a synonym for '1' and LOW means the same as '0'?*




NOW, we are well on our way to building a general purpose table-lookup device.


We can build a 2-dimensional ARRAY of decoders and selectors as follows ...

# Read-only Memory (ROM)

## Full Adder

 


A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Each column is large fan-in "NOR." Note location of pulldowns correspond to a "1" output in the truth table!

Shared decoder

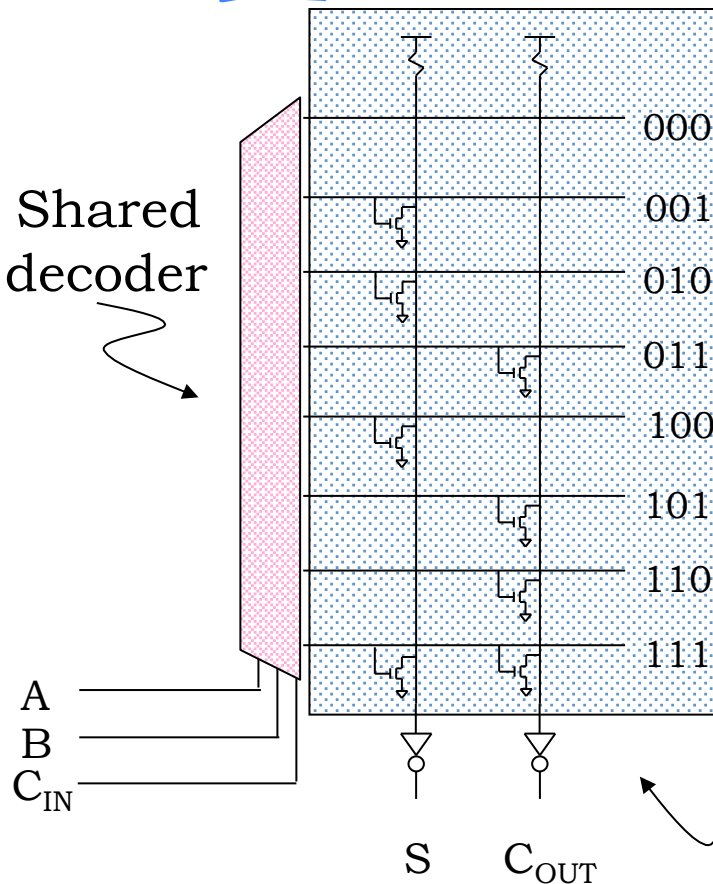


For K inputs, decoder produces  $2^K$  signals, only 1 of which is asserted at a time -- think of it as one signal for each possible product term.


One column for each output

# Read-only Memory (ROM)


## Full Adder

 

A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

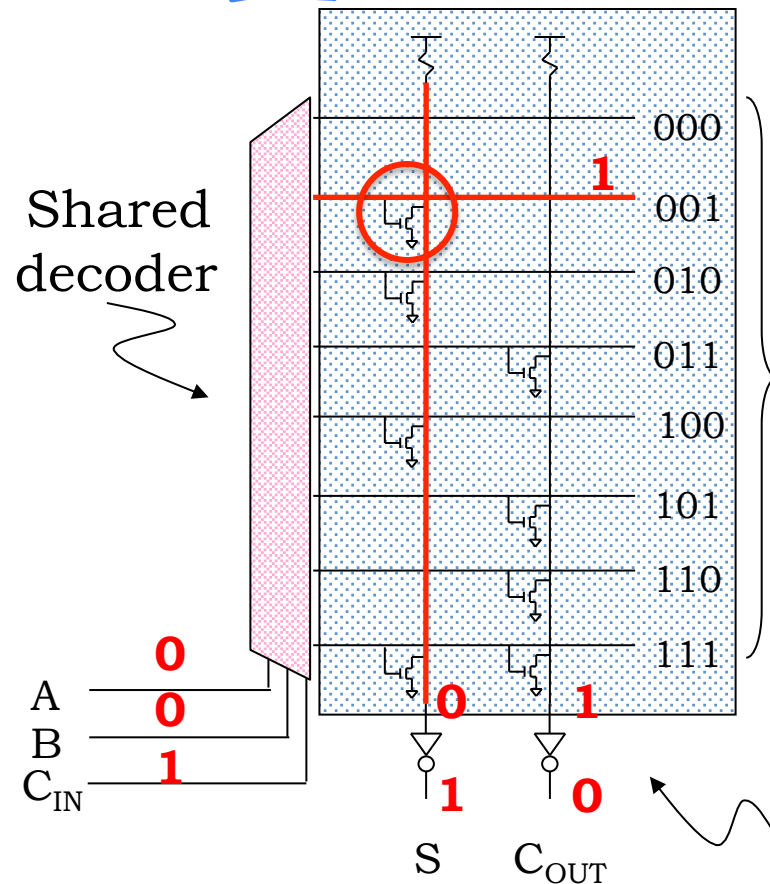Each column is large fan-in "NOR." Note location of pulldowns correspond to a "1" output in the truth table!




For K inputs, decoder produces  $2^K$  signals, only 1 of which is asserted at a time -- think of it as one signal for each possible product term.


One column for each output

# Read-only Memory (ROM)

## Full Adder

 


A	B	$C_i$	S	$C_o$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

*LONG LINES slow down propagation times...*

 The best way to improve this is to build *square arrays*, using some inputs to drive output selectors (MUXes):



**2D Addressing: Standard for ROMs, RAMs, logic arrays...**

# Logic According to ROMs

ROMs *ignore* the structure of combinational functions ...

- Size, layout, and design are independent of function
- Any Truth table can be “programmed” by minor reconfiguration:

- Metal layer (masked ROMs)
- Fuses (Field-programmable PROMs)
- Charge on floating gates (EPROMs)
- ... etc.

ROMs tend to generate “glitchy” outputs. WHY?

Model: LOOK UP value of function in truth table...

Inputs: “ADDRESS” of a T.T. entry

ROM SIZE = # TT entries...

... for an N-input boolean function, size  $\approx$   $2^N \times \text{\#outputs}$

# Summary

- Sum of products
  - Any function that can be specified by a truth table or, equivalently, in terms of AND/OR/NOT (Boolean expression)
  - “3-level” implementation of any logic function
    - Limitations on number of inputs (fan-in) increases depth
  - SOP implementation methods
    - NAND-NAND, NOR-NOR
- Muxes used to build table-lookup implementations
  - Easy to change implemented function -- just change constants
- ROMs
  - Decoder logic generates all possible product terms
  - Selector logic determines which terms are ORed together