

8. Design Tradeoffs

6.004x Computation Structures
Part 1 – Digital Circuits


Copyright © 2015 MIT EECS

Optimizing Your Design

There are a large number of implementations of the same functionality -- each represents a different point in the area-time-power space

Optimization metrics:

 1. Area of the design
2. Throughput
3. Latency
4. Power consumption
5. Energy of executing a task
6. ...



©Advanced Micro Devices (with permission)


VS.



JustinI4 (CC BY-SA 4.0)

CMOS Static Power Dissipation


MOSFET

 

- 1 Tunneling current through gate oxide: SiO_2 is a very good insulator, but when very thin ($< 20\text{\AA}$) electrons can tunnel across.


- 2 Current leakage from drain to source even though MOSFET is “off” (aka sub-threshold conduction)
 - Leakage gets larger as difference between V_{TH} and “off” gate voltage (eg, V_{OL} in an nfet) gets smaller. Significant as V_{TH} has become smaller.
 - Fix: 3D FINFET wraps gate around inversion region

FINFET

 

Irene Ringworm (CC BY-SA 3.0)

CMOS Dynamic Power Dissipation

 


Power dissipated to discharge C:

$$\begin{aligned}
 P_{NFET} &= f_{CLK} \int_0^{t_{CLK}/2} i_{NFET} V_{OUT} dt \\
 &= f_{CLK} C \int_0^{t_{CLK}/2} -C \frac{dV_{OUT}}{dt} V_{OUT} dt \\
 &= f_{CLK} C \int_{V_{DD}}^0 -V_{OUT} dV_{OUT} \\
 &= f_{CLK} C \frac{V_{DD}^2}{2}
 \end{aligned}$$

Power dissipated to recharge C:

$$\begin{aligned}
 P_{PFET} &= f_{CLK} \int_{t_{CLK}/2}^{t_{CLK}} i_{PFET} V_{OUT} dt \\
 &= f_{CLK} \int_{t_{CLK}/2}^{t_{CLK}} C \frac{dV_{OUT}}{dt} V_{OUT} dt \\
 &= f_{CLK} C \int_0^{V_{DD}} V_{OUT} dV_{OUT} \\
 &= f_{CLK} C \frac{V_{DD}^2}{2}
 \end{aligned}$$

CMOS Dynamic Power Dissipation

 

Power dissipated

$$= f C V_{DD}^2 \text{ per node}$$

$$= f N C V_{DD}^2 \text{ per chip}$$

where

f = frequency of charge/discharge

N = number of changing nodes/chip

“Back of the envelope”:

$f \sim 1\text{GHz} = 1e9 \text{ cycles/sec}$

$N \sim 1e8 \text{ changing nodes/cycle}$

$C \sim 1\text{fF} = 1e-15 \text{ farads/node}$

$V \sim 1\text{V}$



$\Rightarrow 100 \text{ Watts}$

trends




How Can We Reduce Power?

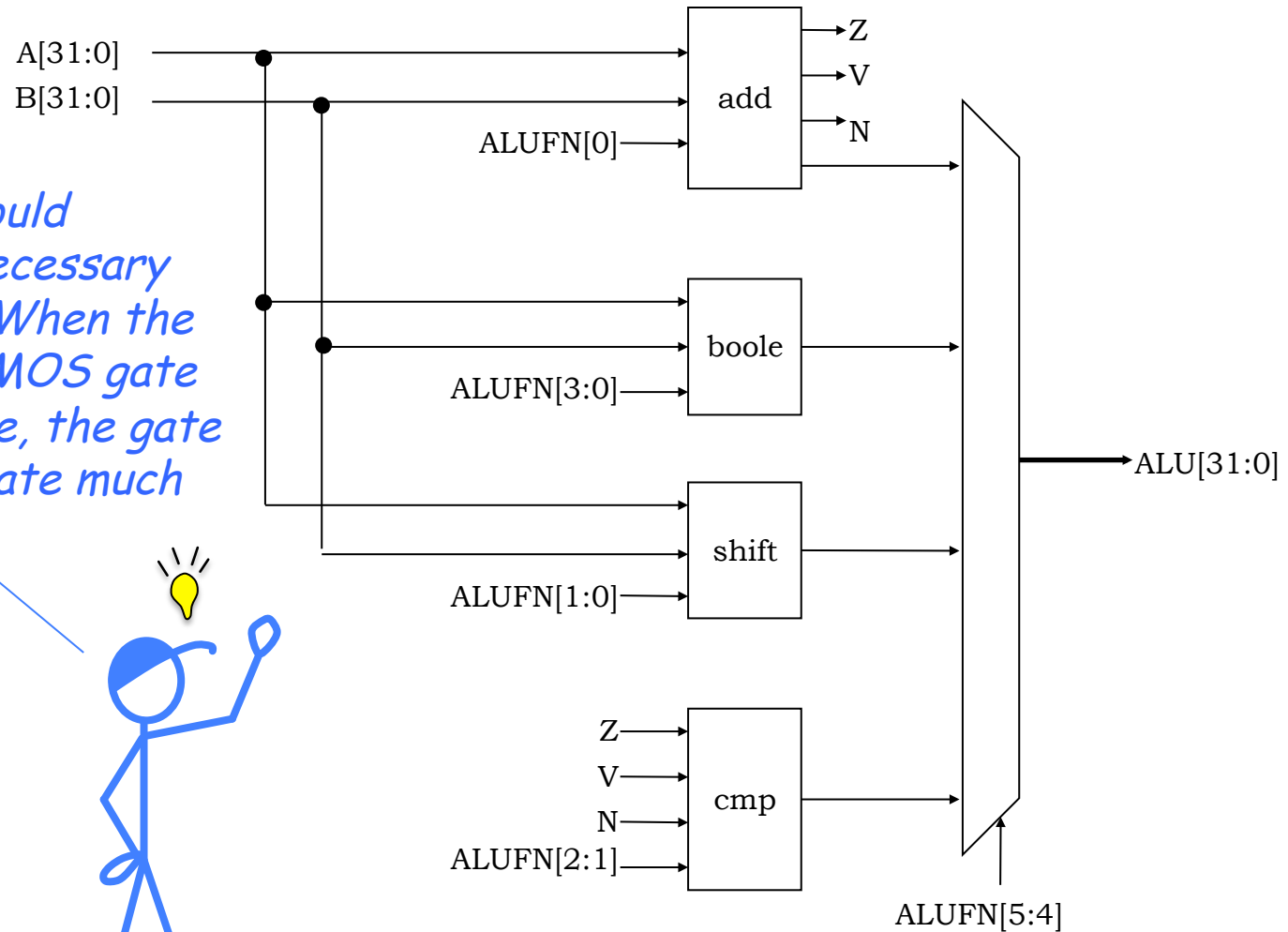 What if we could eliminate unnecessary transitions? When the output of a CMOS gate doesn't change, the gate doesn't dissipate much power!




Fewer Transitions → Lower Power

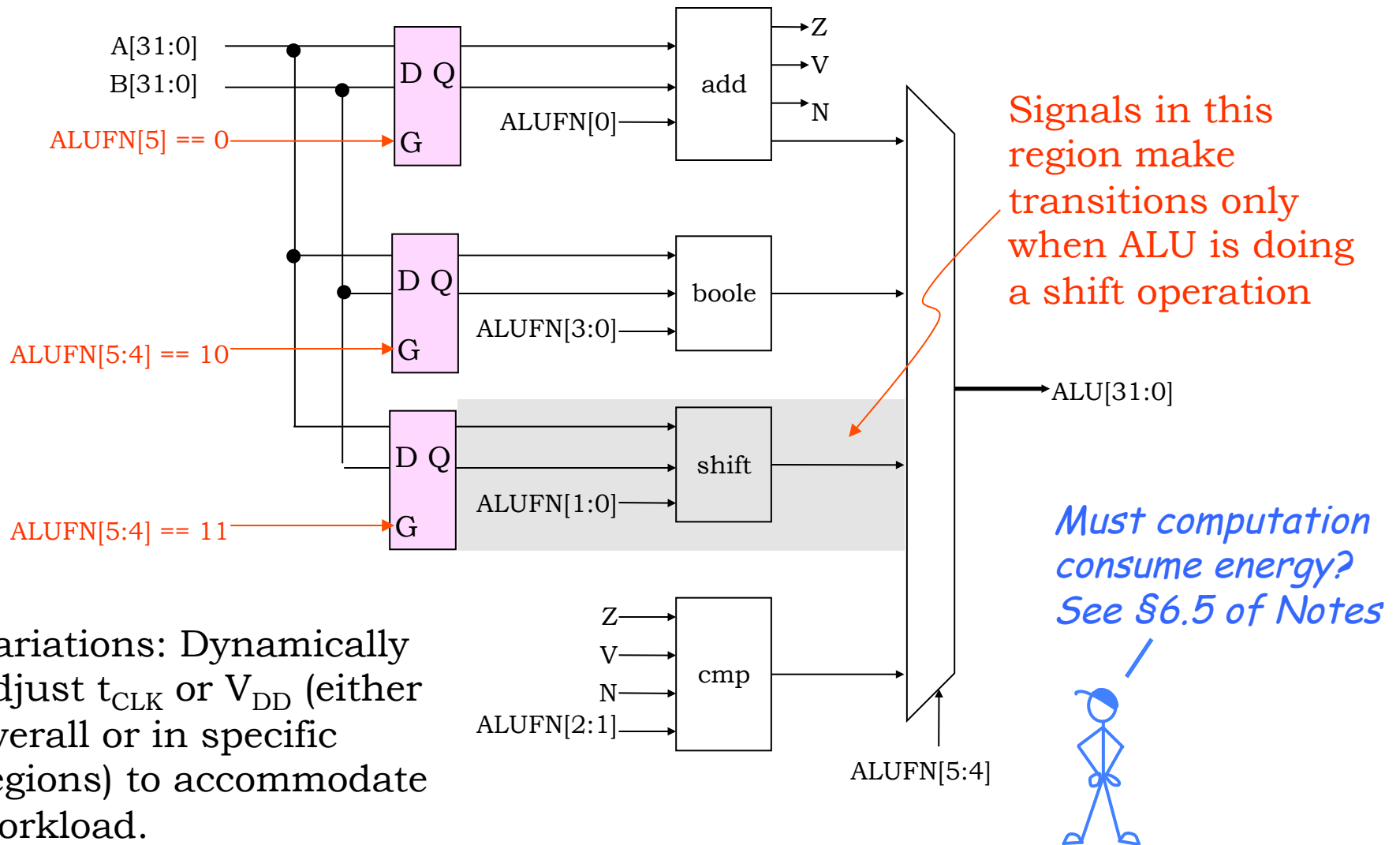

Variations: Dynamically adjust t_{CLK} or V_{DD} (either overall or in specific regions) to accommodate workload.

Improving Speed: Adder Example

 

Worse-case path: carry propagation from LSB to MSB, e.g., when adding $11\dots111$ to $00\dots001$.

$$t_{PD} = (N-1) \cdot \underbrace{(t_{PD,NAND3} + t_{PD,NAND2})}_{CI \text{ to } CO} + \underbrace{t_{PD,XOR}}_{CI_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$

$\Theta(N)$ is read “order N” and tells us that the latency of our adder grows in proportion to the number of bits in the operands.

Performance/Cost Analysis


“Order Of” notation:

"g(n) is of order f(n)" $g(n) = \Theta(f(n))$

$g(n) = \Theta(f(n))$ if there exist $C_2 \geq C_1 > 0$
such that for all but finitely many
integral $n \geq 0$

$$C_1 \cdot f(n) \leq g(n) \leq C_2 \cdot f(n)$$

 $\Theta(\dots)$ implies both
inequalities;
 $O(\dots)$ implies only
the second.



$$g(n) = O(f(n))$$


Example:

$$n^2 + 2n + 3 = \Theta(n^2)$$

since

$$n^2 < n^2 + 2n + 3 < 2n^2$$


“almost always”

 

Carry Select Adders


Hmm. Can we get the high half of the adder working in parallel with the low half?

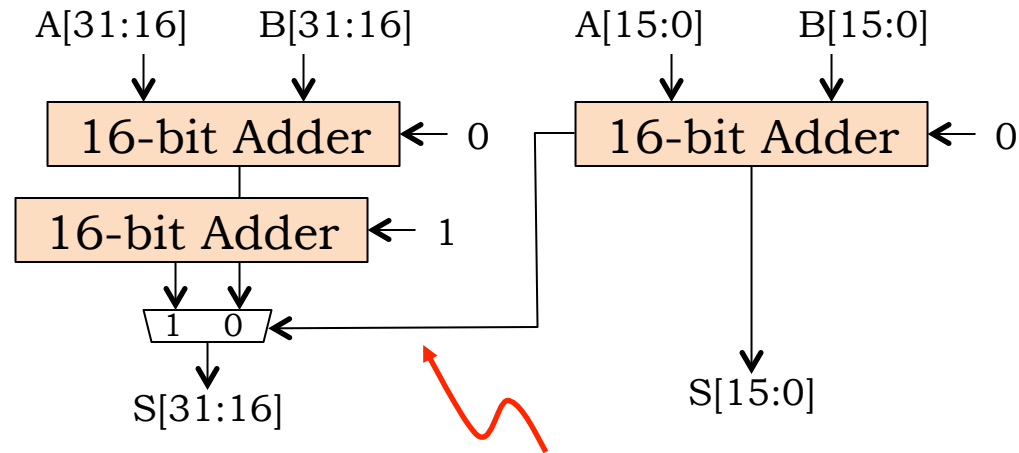Two copies of the high half of the adder: one assumes a carry-in of "0", the other carry-in of "1".



Once the low half computes the actual value of the carry-in to the high half, use it to select the correct version of the high-half addition.

 
$$t_{PD} = 16 * t_{PD, CI \rightarrow CO} + t_{PD, MUX2} \approx \text{half of } 32 * t_{PD, CI \rightarrow CO}$$



Aha! Apply the same strategy to build 16-bit adders from 8-bit adders. And 8-bit adders from 4-bit adders, and so on. Resulting t_{PD} for N-bit adder is $\Theta(\log N)$.

32-bit Carry Select Adder

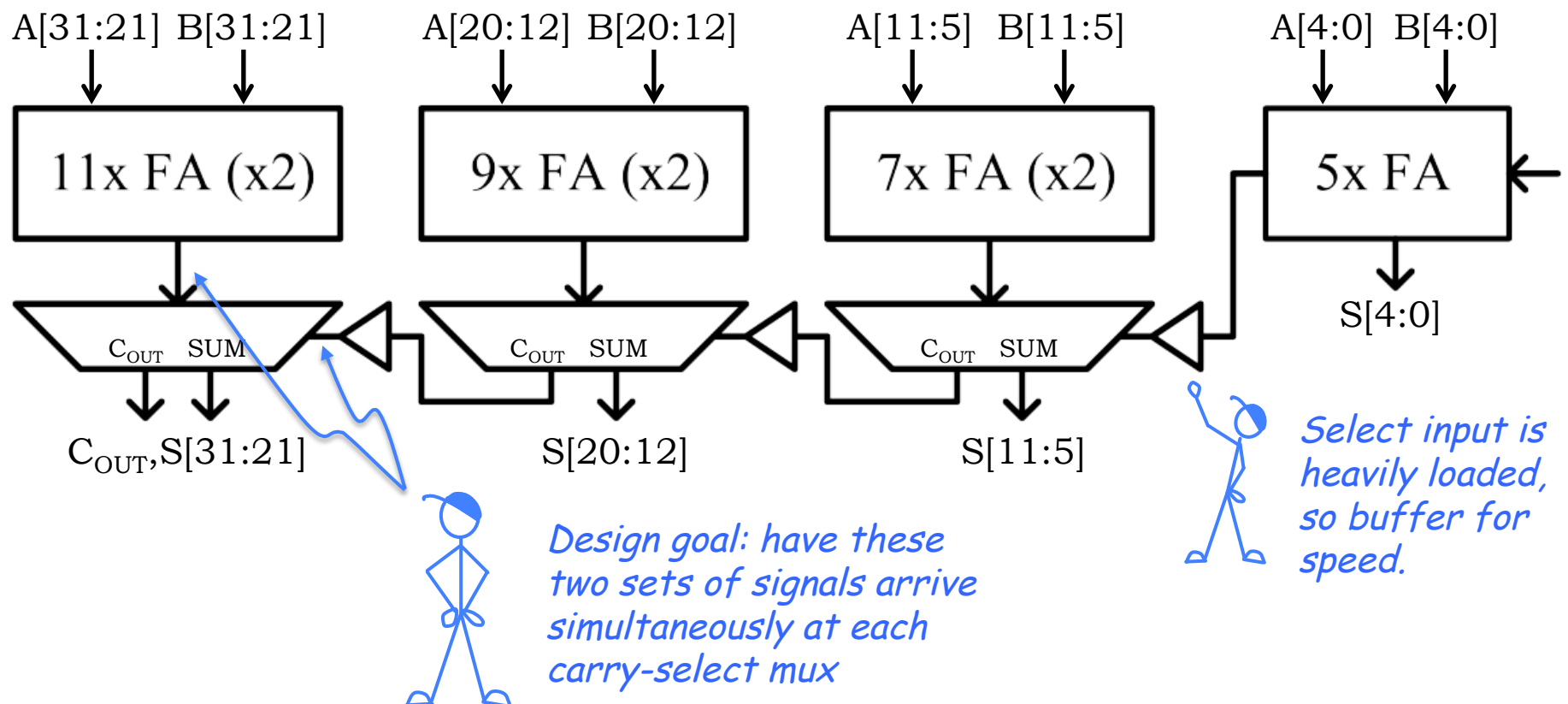Practical Carry-select addition: choose block sizes so that trial sums and carry-in from previous stage arrive simultaneously at MUX.



Wanted: Faster Carry Logic!


Let's see if we can improve the speed by rewriting the equations for C_{OUT} :

$$\begin{aligned}C_{OUT} &= AB + AC_{IN} + BC_{IN} \\ &= AB + (A + B)C_{IN} \\ &= \mathbf{G} + \mathbf{P} C_{IN} \quad \text{where } G = AB \text{ and } P = A + B\end{aligned}$$


\nearrow generate \nearrow propagate

Actually, P is usually defined as $P = A \oplus B$ which won't change C_{OUT} but will allow us to express S as a simple function of P and C_{IN} :

$$S = P \oplus C_{IN}$$

 

 *CO logic using only
3 NAND2 gates!
Think I'll borrow
that for my FA
circuit!*




Carry Look-ahead Adders (CLA)

We can build a hierarchical carry chain by generalizing our definition of the Carry Generate/Propagate (GP) Logic. We start by dividing our addend into two parts, a higher part, H, and a lower part, L. The GP function can be expressed as follows:

$$G_{HL} = G_H + P_H G_L$$


$$P_{HL} = P_H P_L$$

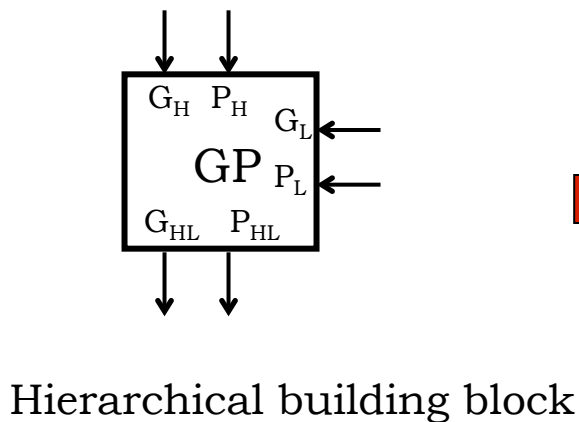Generate a carry out if the high part generates one, or if the low part generates one and the high part propagates it.
 Propagate a carry if both the high and low parts propagate theirs.




P/G generation

1st level of lookahead

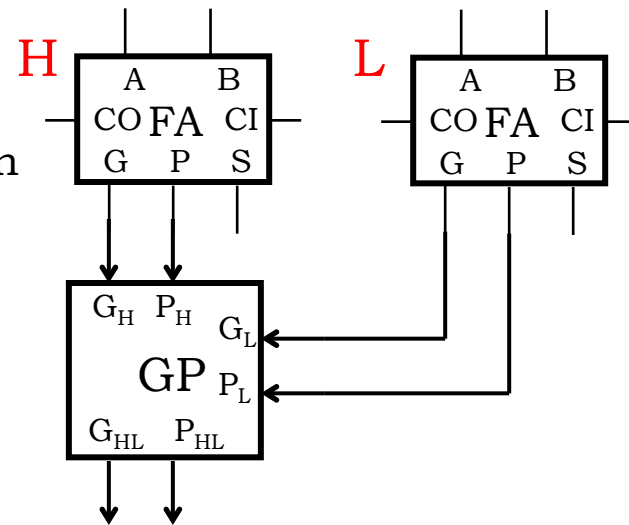


8-bit CLA (generate G & P)

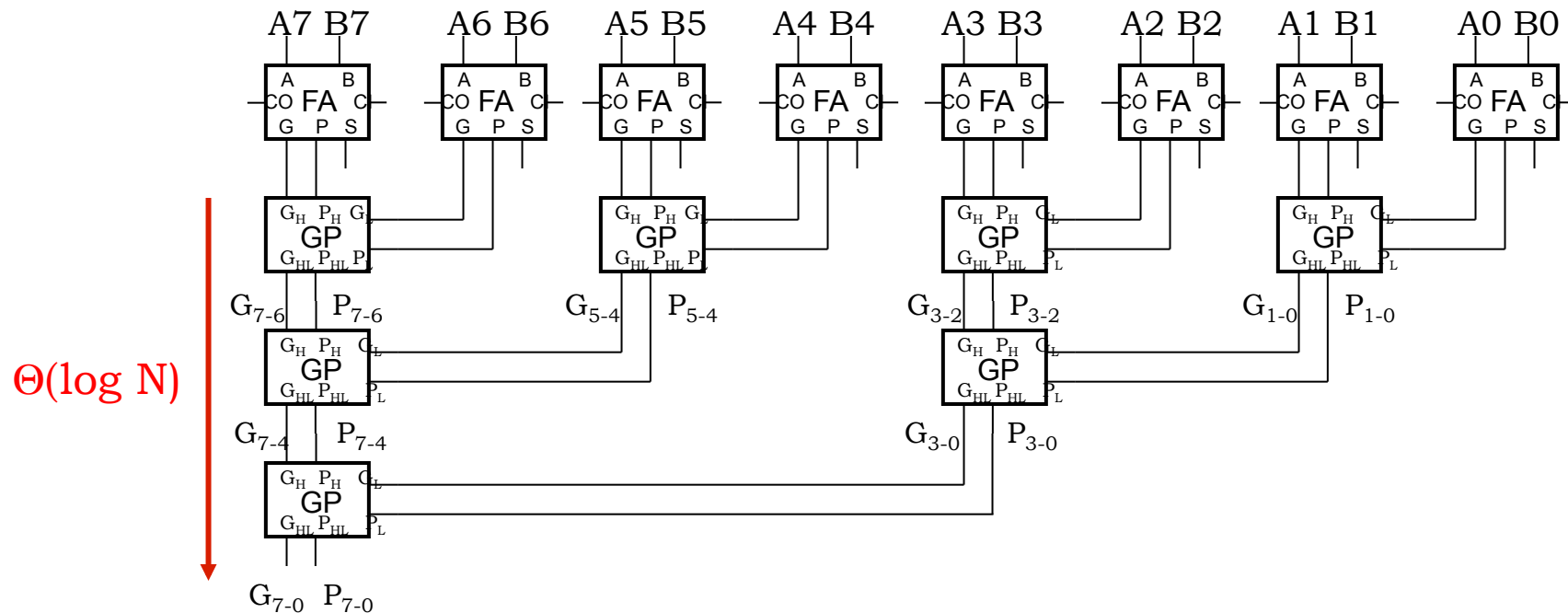


We can build a tree of GP units to compute the generate and propagate logic for any sized adder. Assuming N is a power of 2, we'll need $N-1$ GP units.

This will let us to quickly compute the carry-ins for each FA!

8-bit CLA (complete)

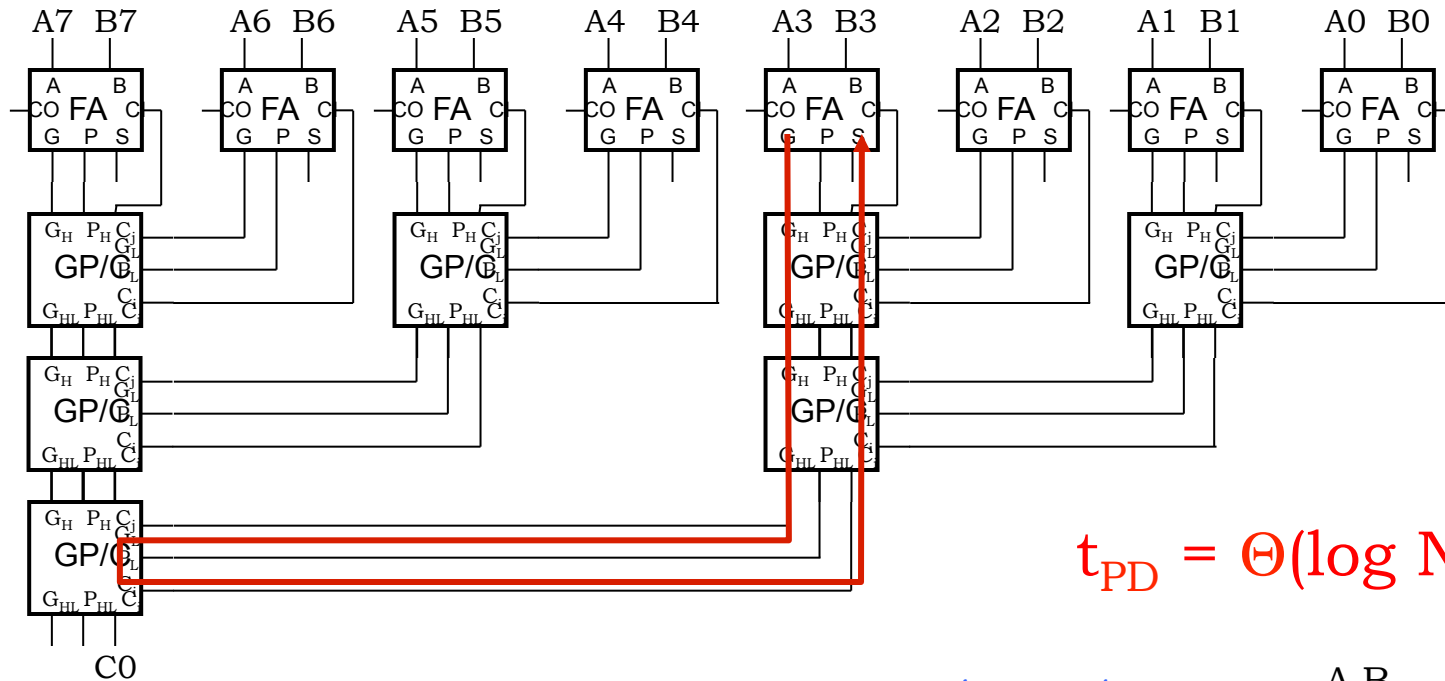


$$t_{PD} = \Theta(\log N)$$

 

To learn more, look up Kogge-Stone adders on Wikipedia.

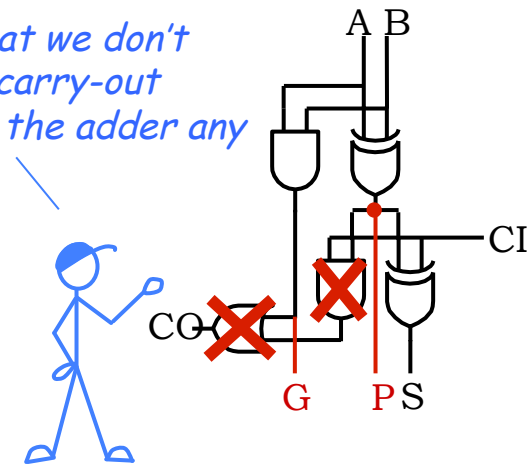Notice that we don't need the carry-out output of the adder any more.



Binary Multiplication*

The "Binary"
Multiplication
Table

*	0	1
0	0	0
1	0	1

Hey, that
looks like
an AND
gate



* Actually unsigned binary multiplication

$$\begin{array}{r} A_3 \quad A_2 \quad A_1 \quad A_0 \\ \times B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$


AB_i called a "partial product" \longrightarrow

$$\begin{array}{r} A_3B_0 \quad A_2B_0 \quad A_1B_0 \quad A_0B_0 \\ A_3B_1 \quad A_2B_1 \quad A_1B_1 \quad A_0B_1 \\ A_3B_2 \quad A_2B_2 \quad A_1B_2 \quad A_0B_2 \\ + A_3B_3 \quad A_2B_3 \quad A_1B_3 \quad A_0B_3 \\ \hline \end{array}$$

Multiplying N-digit number by M-digit number gives (N+M)-digit result


Easy part: forming partial products (just an AND gate since B_i is either 0 or 1)
Hard part: adding M N-bit partial products

Combinational Multiplier

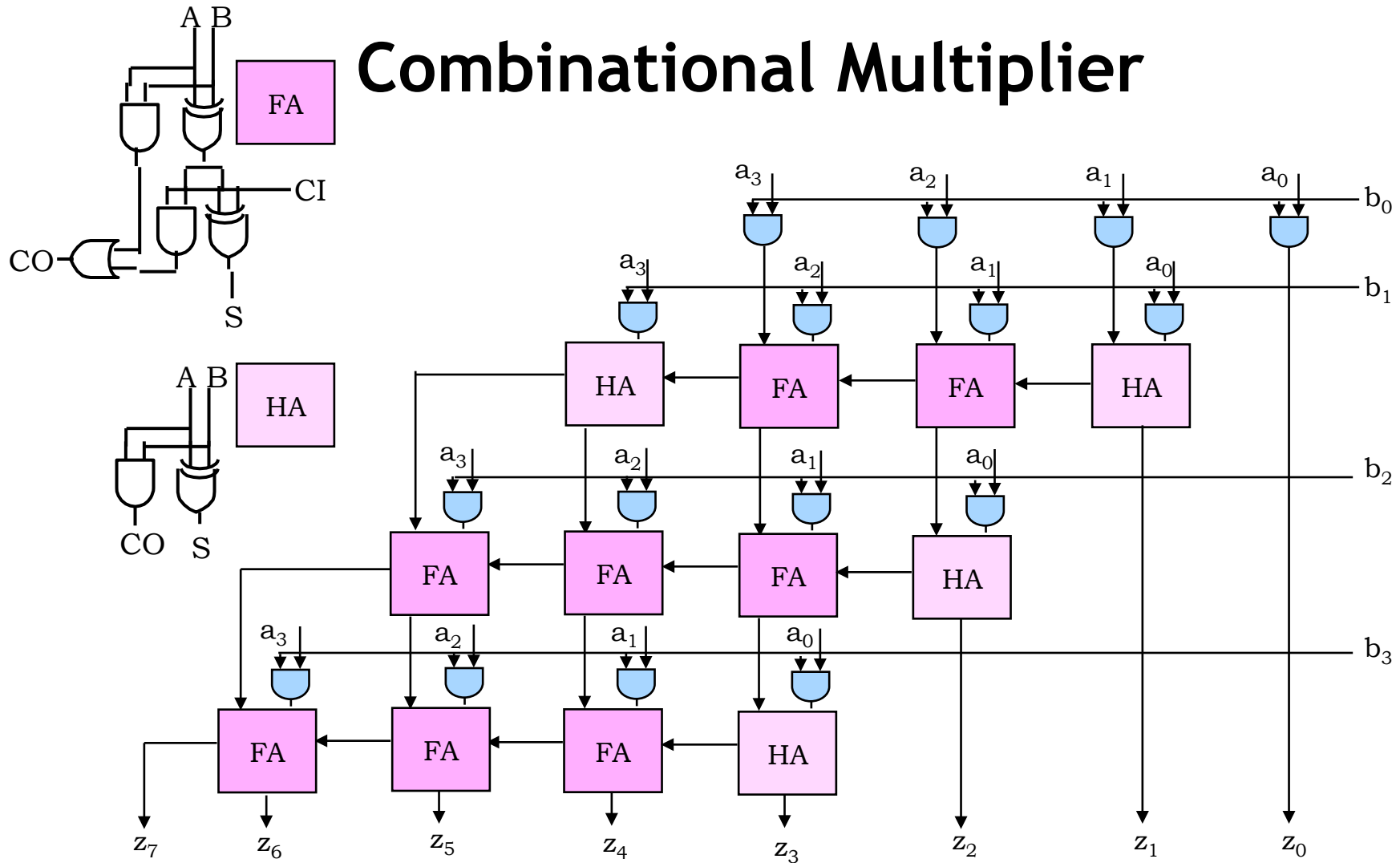


Latency = $\Theta(N)$
 Throughput = $\Theta(1/N)$
 Hardware = $\Theta(N^2)$

2's Complement Multiplier

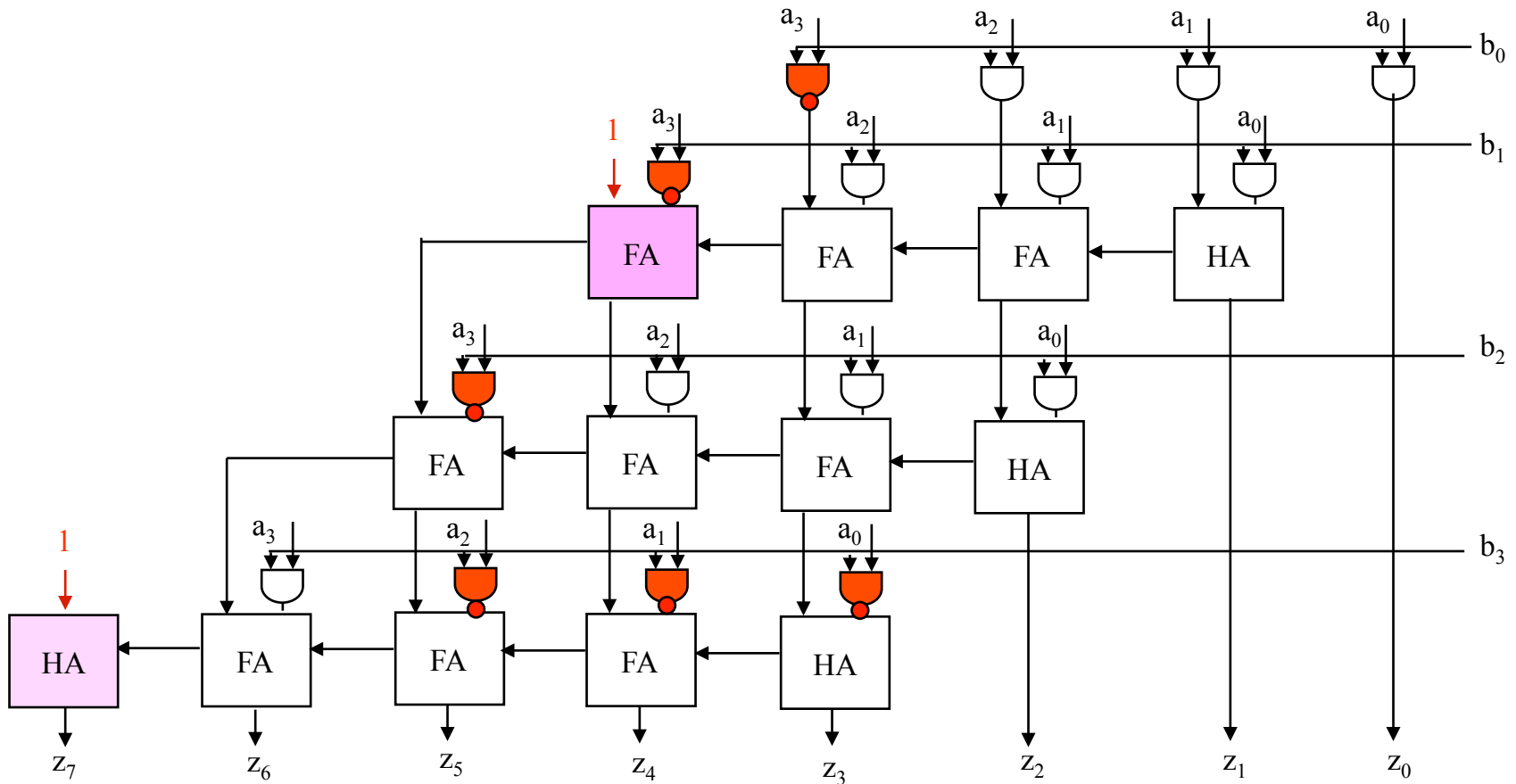

Increase Throughput With Pipelining

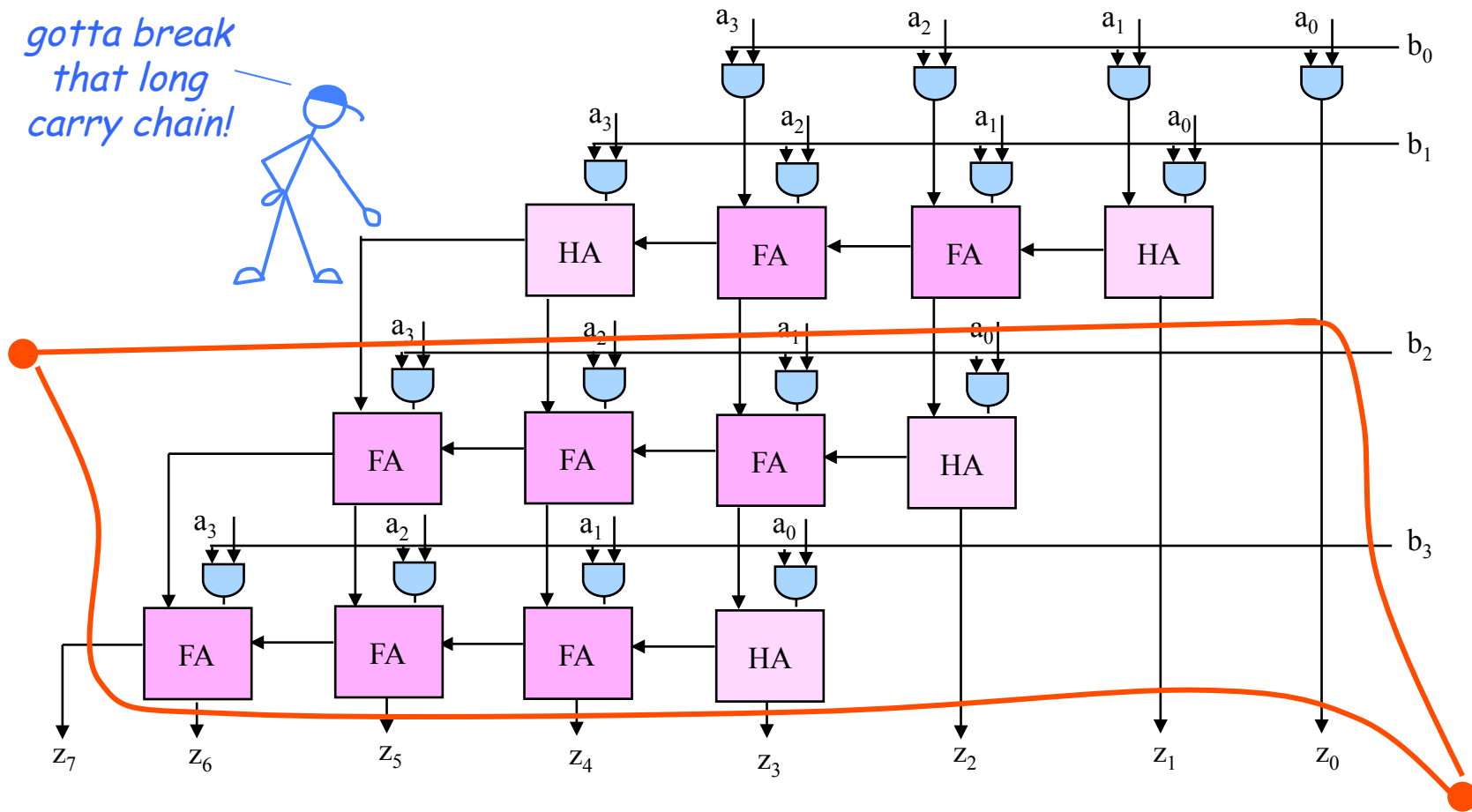


Before pipelining: Throughput = $\sim 1/(2N) = \Theta(1/N)$

After pipelining: Throughput = $\sim 1/N = \Theta(1/N)$


“Carry-save” Pipelined Multiplier

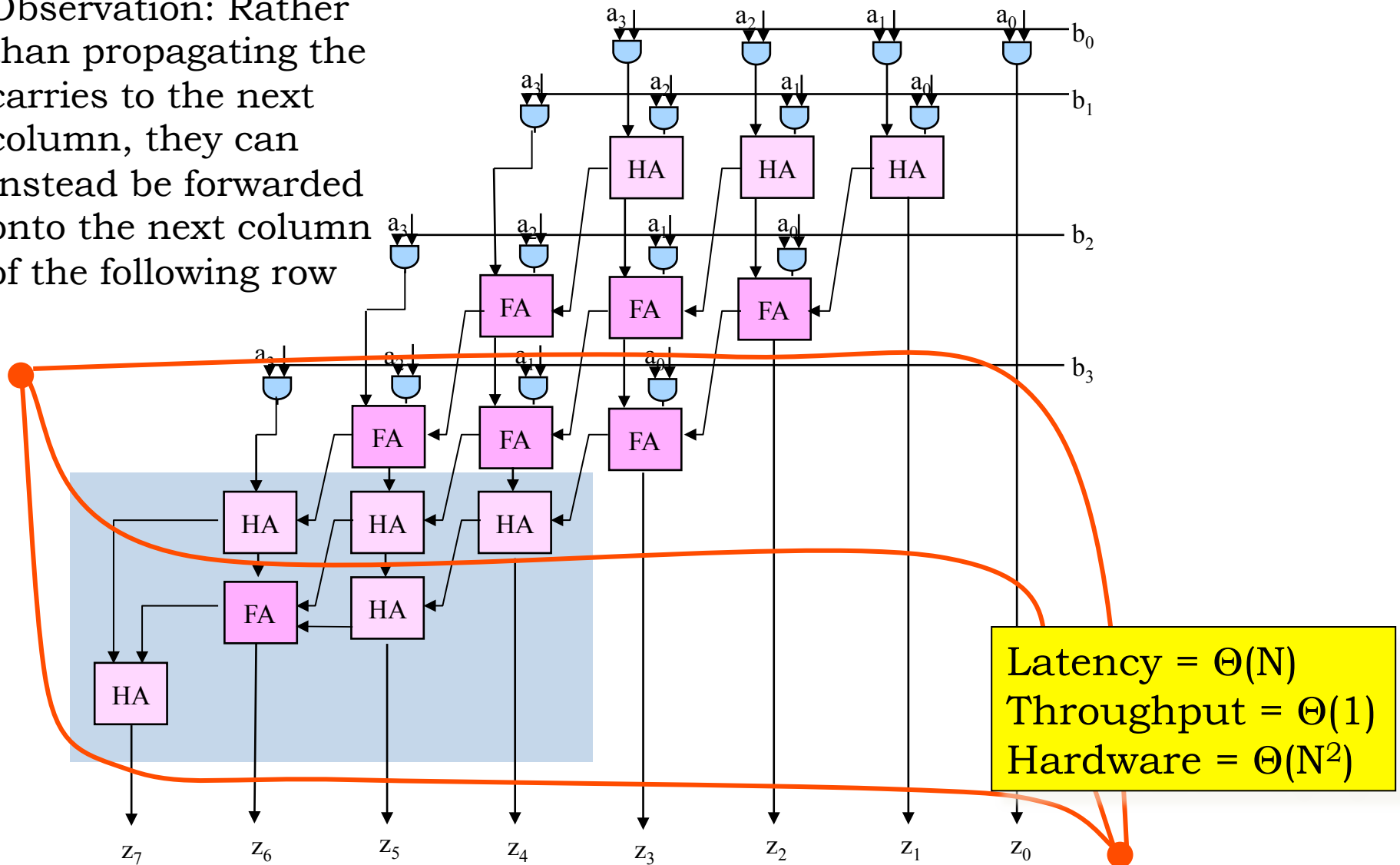Observation: Rather than propagating the carries to the next column, they can instead be forwarded onto the next column of the following row



Reduce Area With Sequential Logic

 Assume the multiplicand (A) has N bits and the multiplier (B) has M bits. If we only want to invest in a single N-bit adder, we can build a sequential circuit that *processes a single partial product at a time* and then cycle the circuit M times:



Init: $P \leftarrow 0$, load A&B

```
Repeat M times {
  P ← P + (BLSB==1 ? A : 0)
  shift SN,P,B right one bit
}
```

Done: (N+M)-bit result in P,B

*N+1 Sum bits and
N saved carries*

Latency = $\Theta(N)$
Throughput = $\Theta(1/N)$
Hardware = $\Theta(N)$

$T_{PD} = \Theta(1)$ for carry-save (see previous slide),
but adds $\Theta(N)$ cycles & $\Theta(N)$ hardware

Summary

- Power dissipation can be controlled by dynamically varying T_{CLK} , V_{DD} or by selectively eliminating unnecessary transitions.
- Functions with N inputs have minimum latency of $O(\log N)$ if output depends on all the inputs. But it can take some doing to find an implementation that achieves this bound.
- Performing operations in “slices” is a good way to reduce hardware costs (but latency increases)
- Pipelining can increase throughput (but latency increases)
- Asymptotic analysis only gets you so far – factors of 10 matter in real life and typically N isn't a parameter that's changing within a given design.