 


# 13. Building the Beta


6.004x Computation Structures  
Part 2 – Computer Architecture

Copyright © 2015 MIT EECS

 
# CPU Design Tradeoffs



Maximum Performance: measured by the numbers of instructions executed per second



 Minimum Cost : measured by the size of the circuit.



Best Performance/Price: measured by the ratio of MIPS to size. In power-sensitive applications MIPS/Watt is important too.


# Processor Performance

- “Iron Law” of performance:


$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}} \qquad \text{Perf} = \frac{1}{\text{Time}}$$

- Options to reduce execution time:
  - Executed instructions ↓ (work/instruction ↑)
  - Cycles per instruction (CPI) ↓
  - Cycle time ↓ (frequency ↑)
- Today: Simple, CPI=1 but low-frequency Beta
  - Later: Pipelining to increase frequency

# Reminder: Beta ISA

 

 Operate class:  $\text{Reg}[R_c] \leftarrow \text{Reg}[R_a] \text{ op } \text{Reg}[R_b]$



Operate class:  $\text{Reg}[R_c] \leftarrow \text{Reg}[R_a] \text{ op } \text{SXT}(C)$

Opcodes, both formats:

ADD	SUB	MUL*	DIV*	*optional
CMPEQ	CMPLE	CMPLT		
AND	OR	XOR	XNOR	
SHL	SHR	SRA		



LD:  $\text{Reg}[R_c] \leftarrow \text{Mem}[\text{Reg}[R_a] + \text{SXT}(C)]$

ST:  $\text{Mem}[\text{Reg}[R_a] + \text{SXT}(C)] \leftarrow \text{Reg}[R_c]$

LDR:  $\text{Reg}[R_c] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SXT}(C)]$

BEQ:  $\text{Reg}[R_c] \leftarrow \text{PC} + 4$ ; if  $\text{Reg}[R_a] = 0$  then  $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$

BNE:  $\text{Reg}[R_c] \leftarrow \text{PC} + 4$ ; if  $\text{Reg}[R_a] \neq 0$  then  $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$

JMP:  $\text{Reg}[R_c] \leftarrow \text{PC} + 4$ ;  $\text{PC} \leftarrow \text{Reg}[R_a]$

Instruction classes distinguished by OPCODE:

OP

OPC

MEM

Control Flow


# Approach: Incremental Featurism

We'll implement datapaths for each instruction class individually, and merge them (using MUXes, etc)

## Steps:

1. ALU instructions
2. Load & store instructions
3. Jump & branch instructions
4. Exceptions

## Component Repertoire:

 




Registers



Muxes





"Black box" ALU

   

Memories

# Multi-Ported Register File

 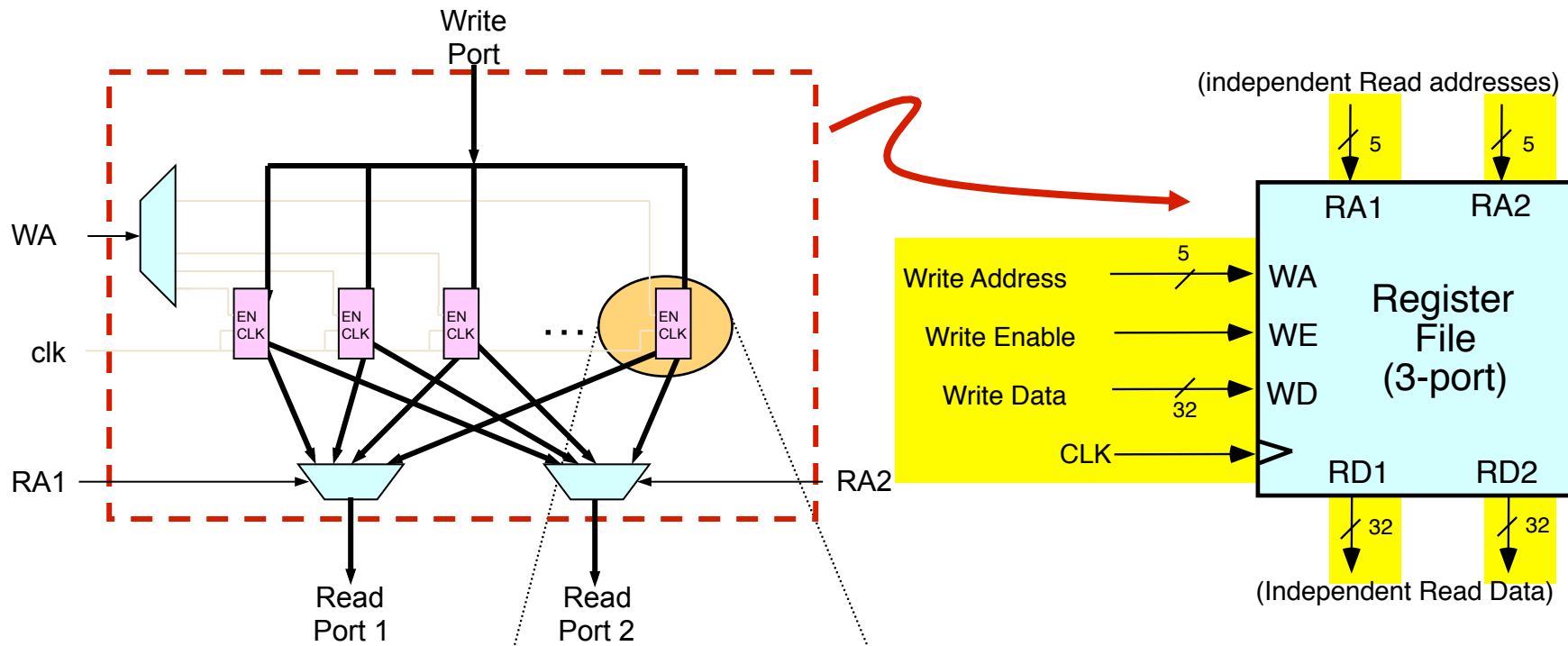


Load-enabled register

2 **combinational** READ ports\*,  
1 **clocked** WRITE port

\*internal logic ensures Reg[31] reads as 0
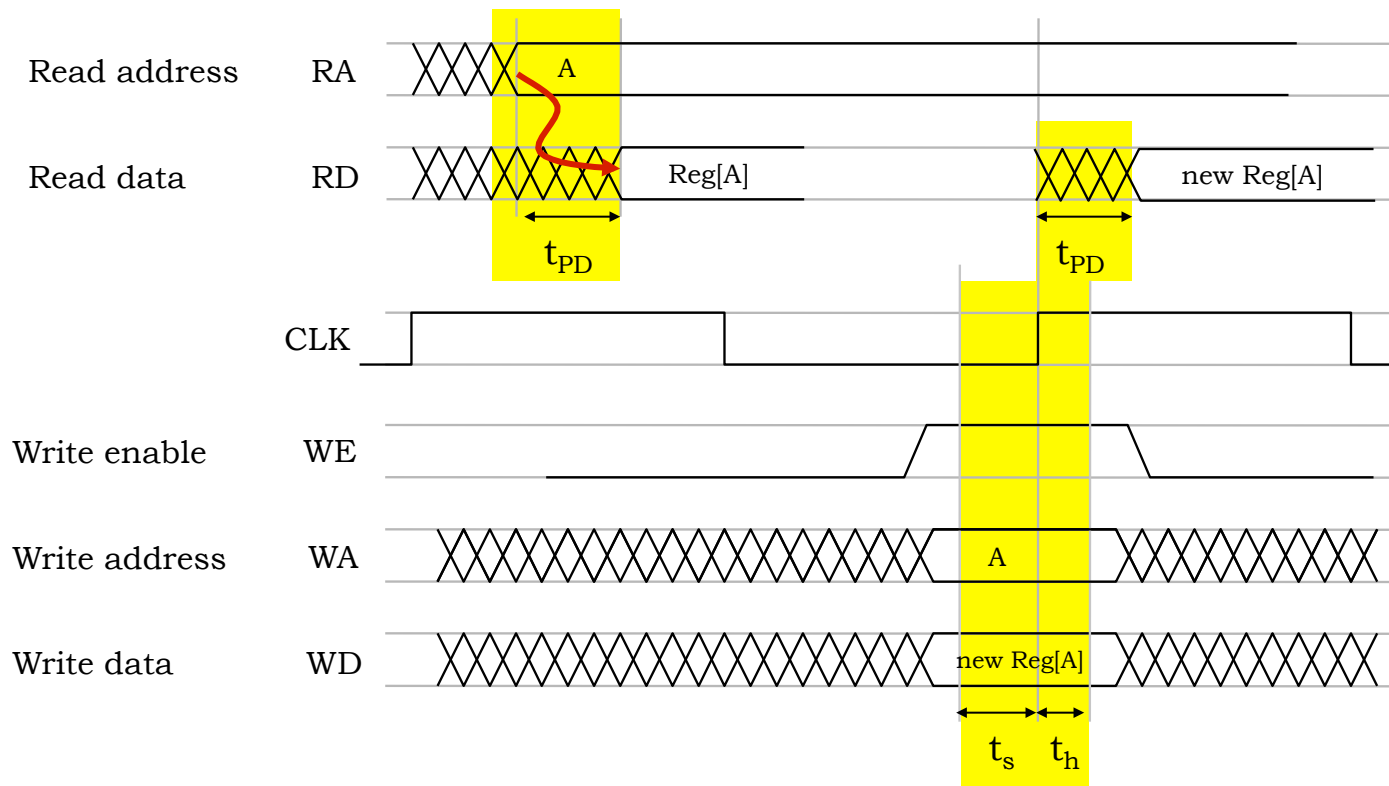
# Register File Timing

2 **combinational** READ ports, 1 **clocked** WRITE port




What if (say)  $WA=RA1$ ???

RD1 reads "old" value of  $Reg[RA1]$  until next clock edge!

# ALU Instructions

32-bit (4-byte) ADD instruction:

 

*Means, to Beta,  $Reg[R4] \leftarrow Reg[R2] + Reg[R3]$*


Need hardware to:

- **FETCH** (read) 32-bit instruction for the current cycle
- **DECODE** instruction: ADD, SUB, XOR, etc
- **READ** operands (Ra, Rb) from Register File
- **EXECUTE** operation
- **WRITE-BACK** result into Register File (Rc)



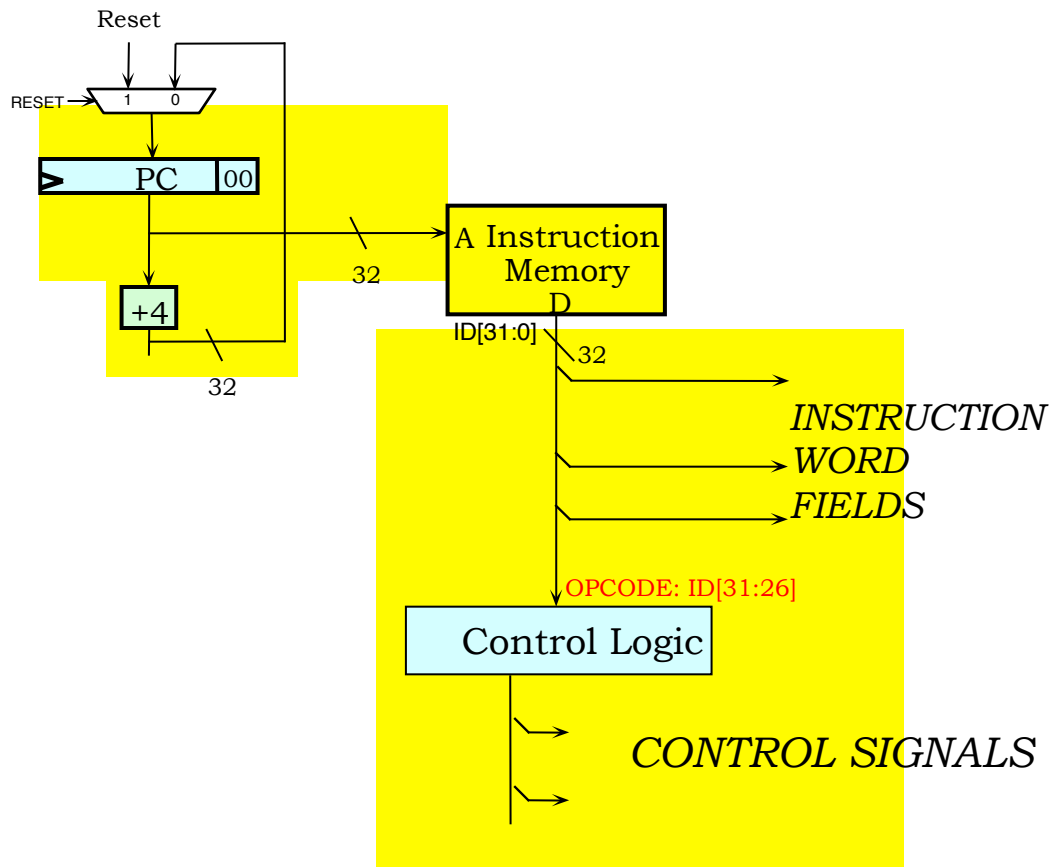
# Instruction Fetch/Decode

Use a counter to FETCH the next instruction: PROGRAM COUNTER (PC)




- Use PC as memory address
- Add 4 to PC, load new value at end of cycle
- Fetch instruction from memory
  - Use some instruction fields directly (register numbers, 16-bit constant)
  - Use bits [31:26] to generate control signals


# ALU Op Datapath

 

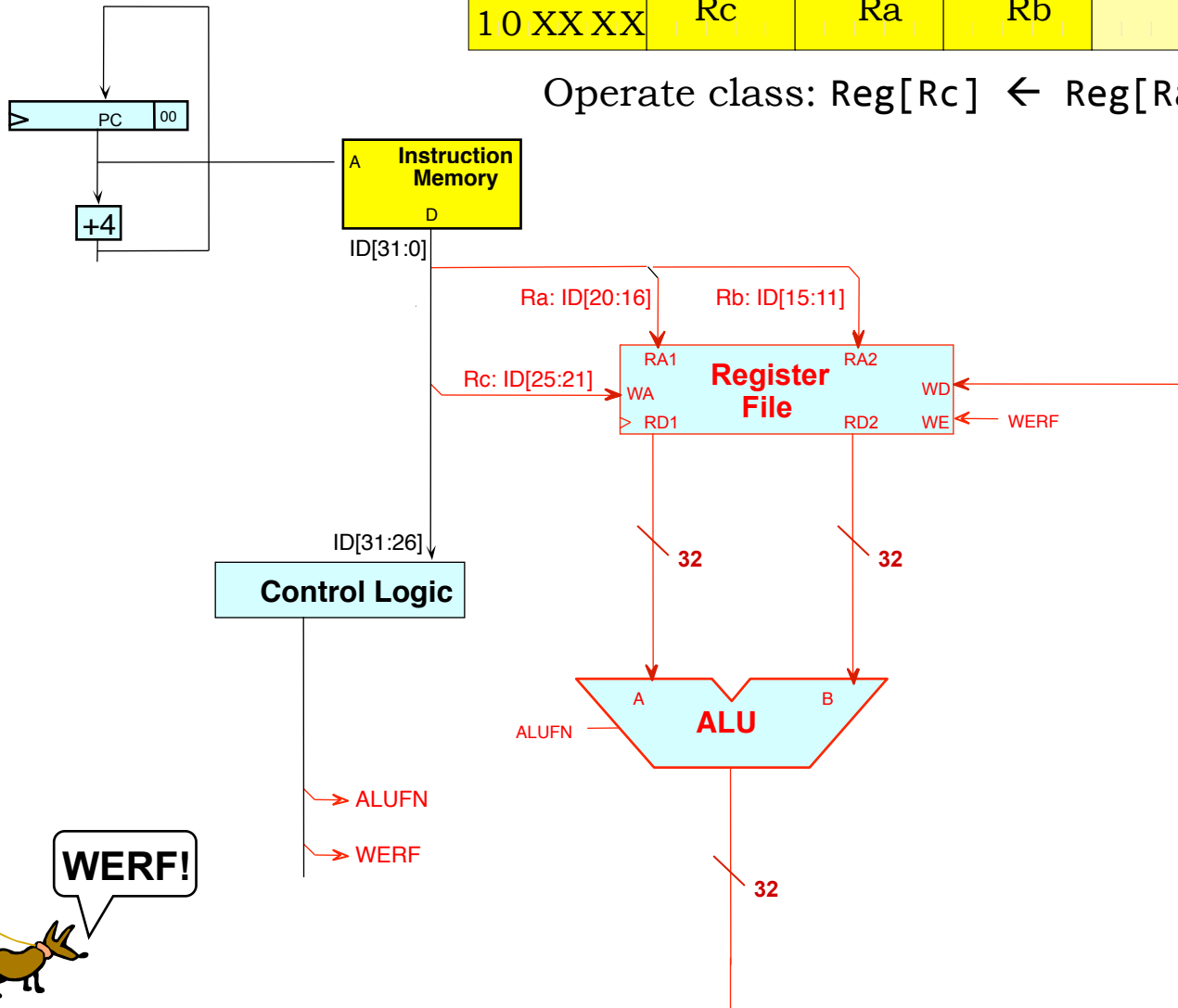
Operate class:  $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$




# ALU Op Datapath

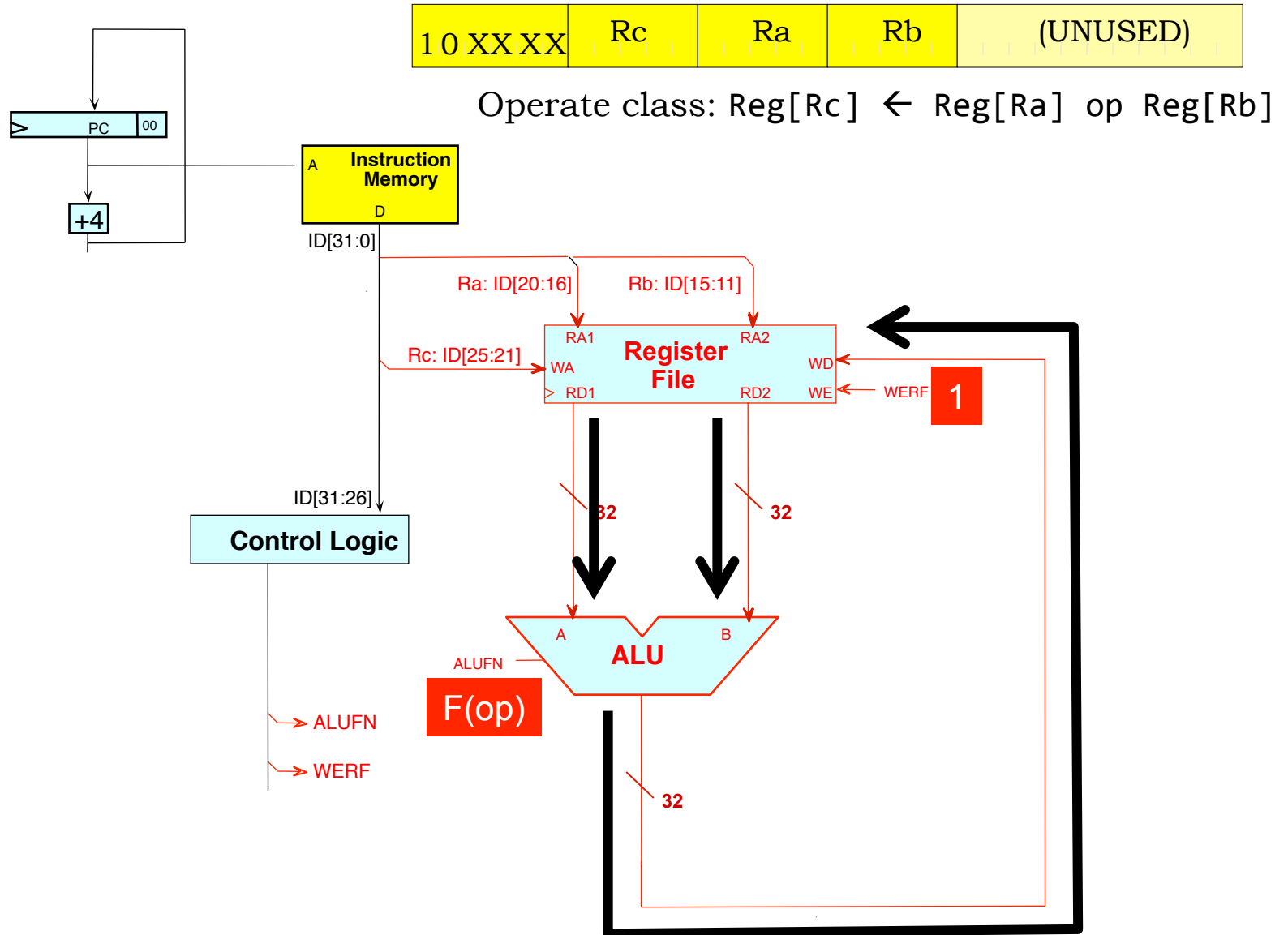

# ALU Operations (with constant)

 

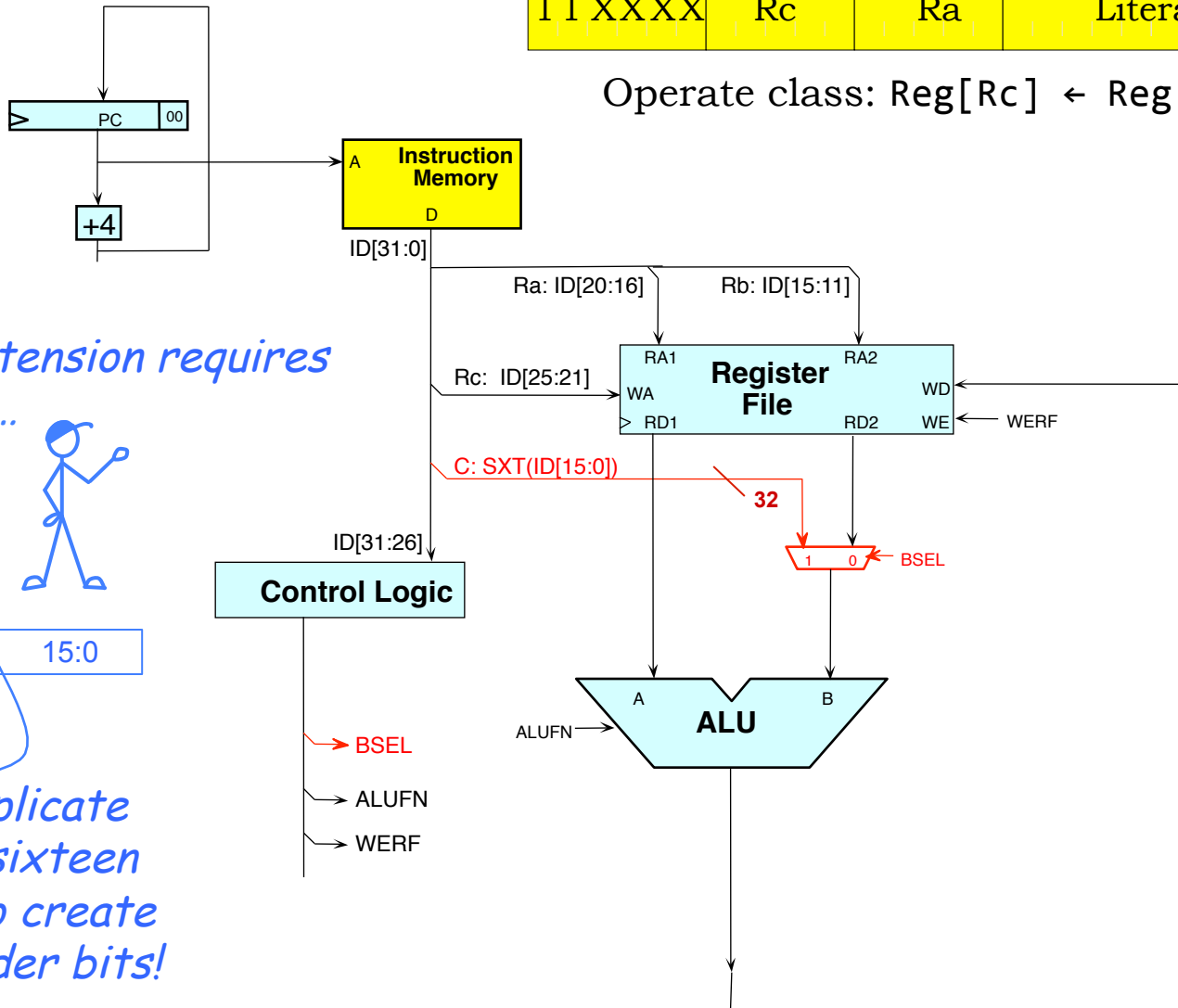Operate class:  $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SXT}(C)$




*Sign-extension requires no logic...*




*Just replicate ID[15] sixteen times to create high-order bits!*


# ALU Operations (with constant)

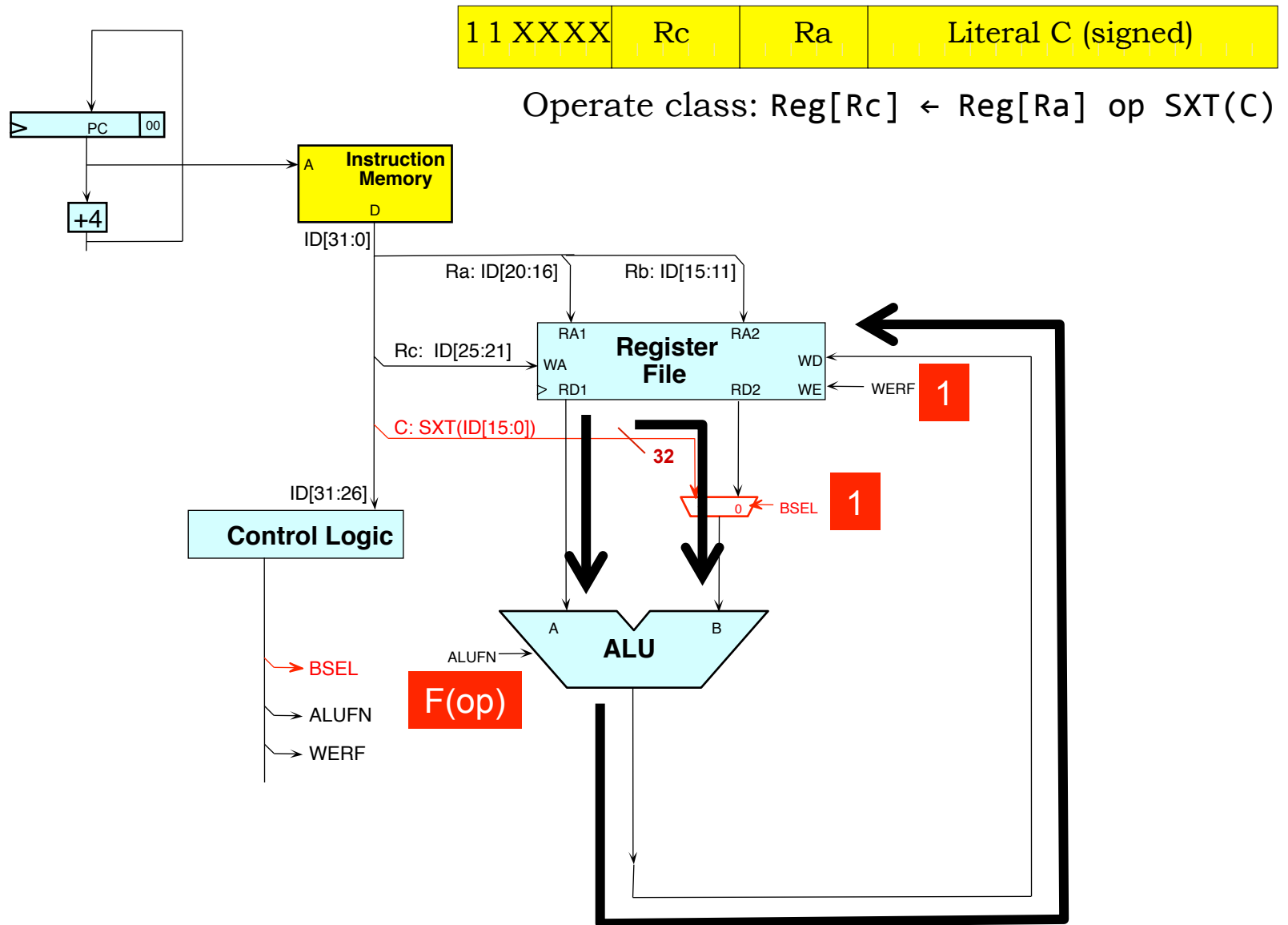


# Load Instruction

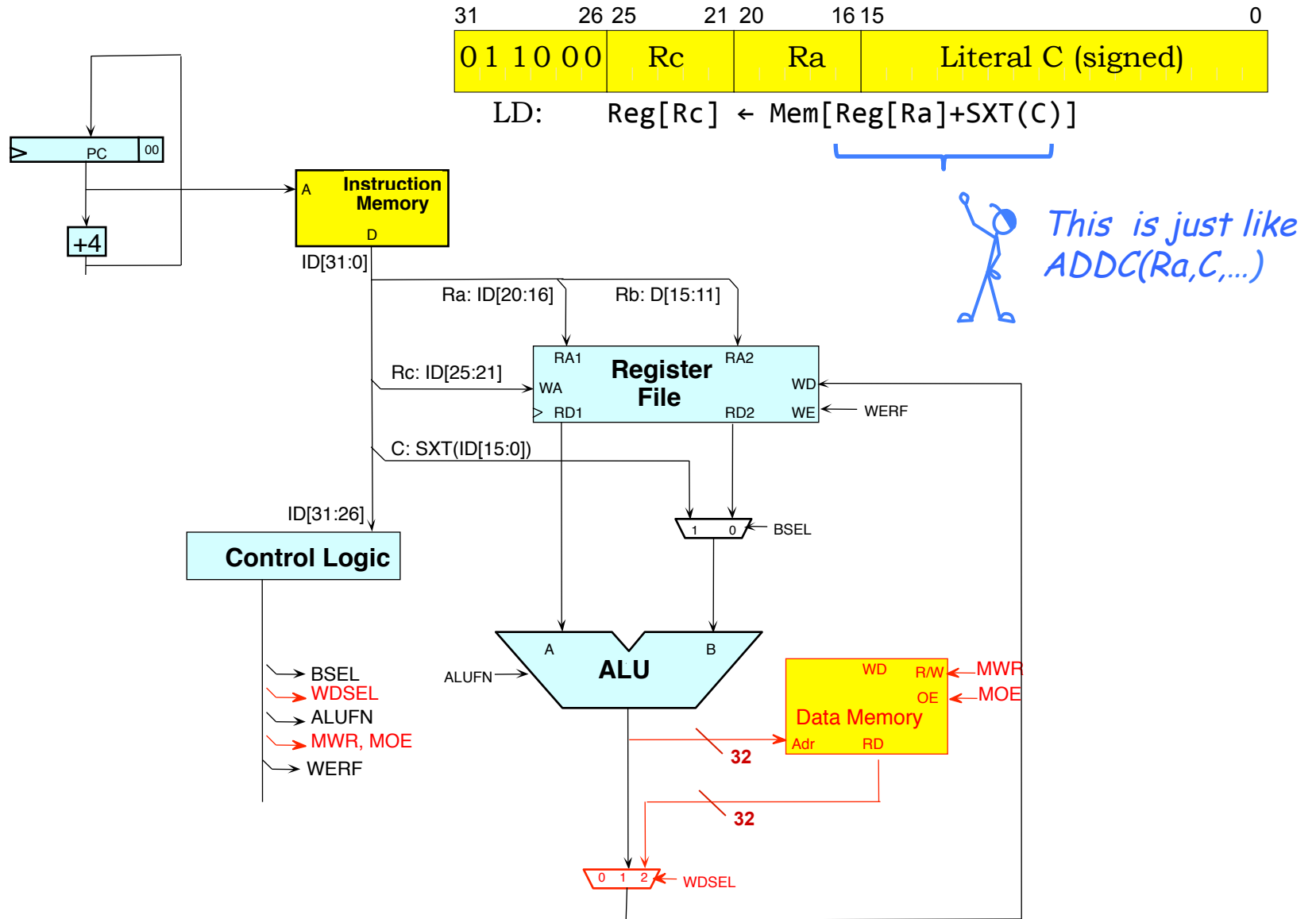


# Load Instruction

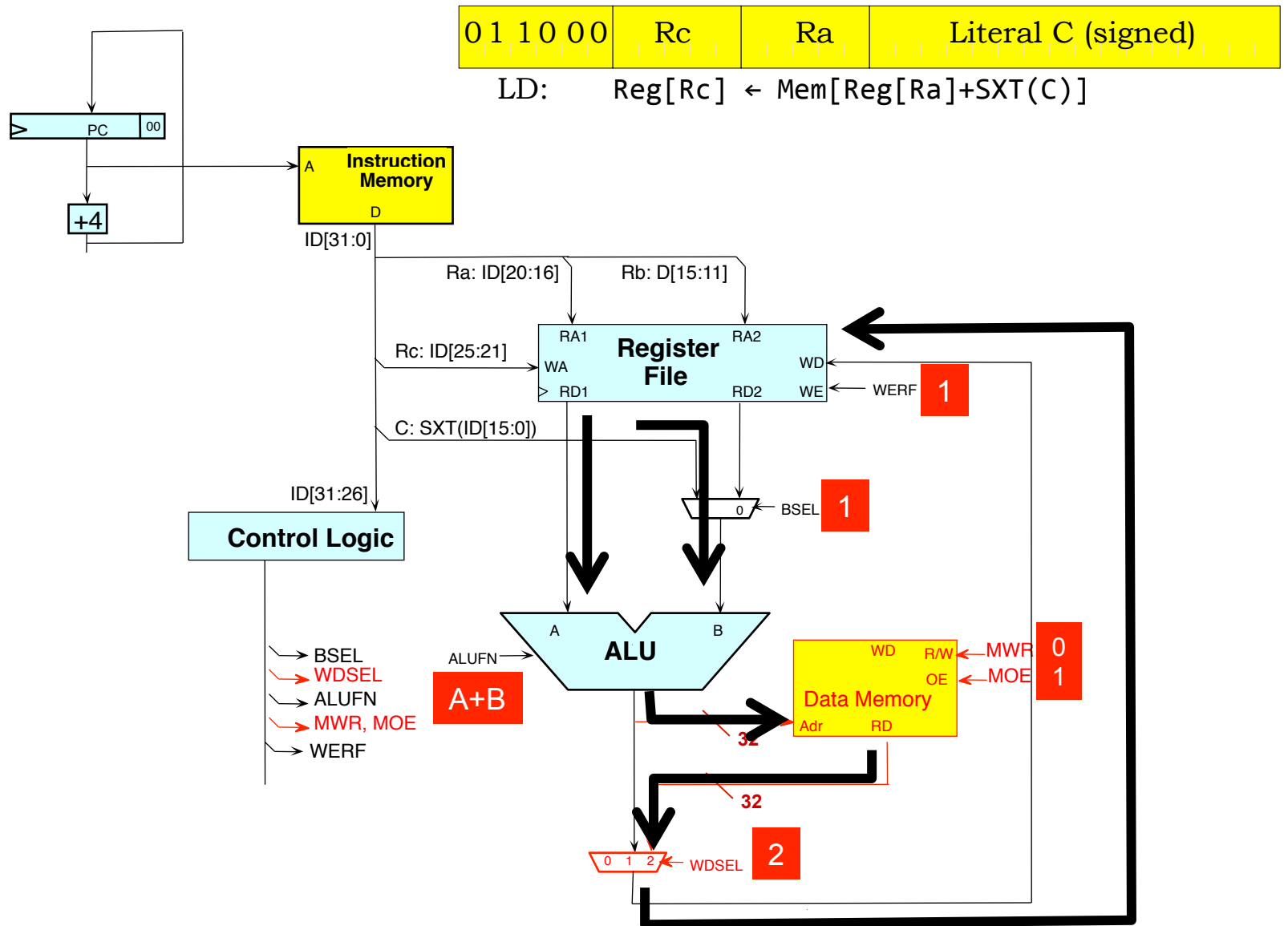

# Store Instruction

 


ST: Mem[Reg[Ra]+SXT(C)] ← Reg[Rc]

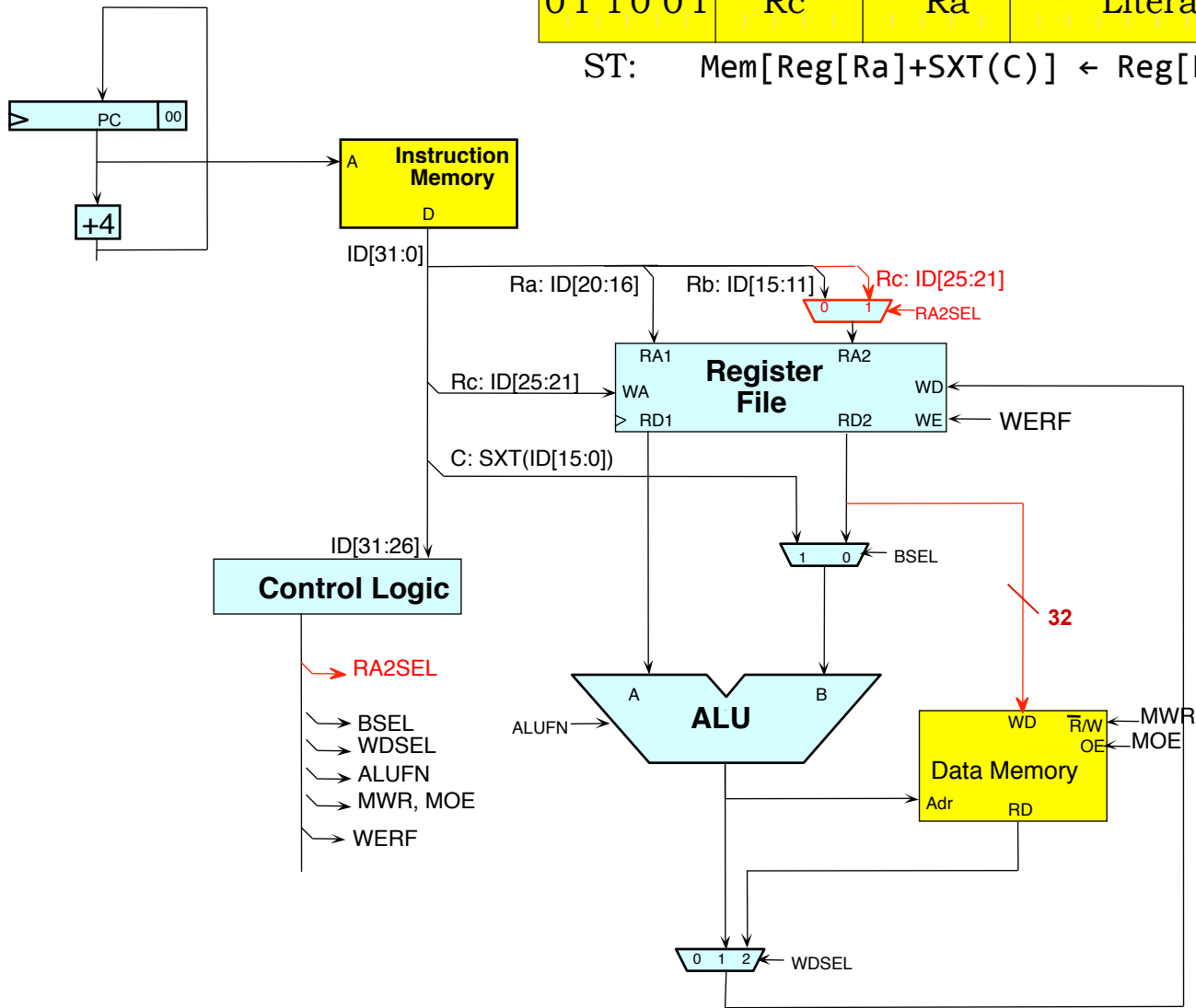




# Store Instruction

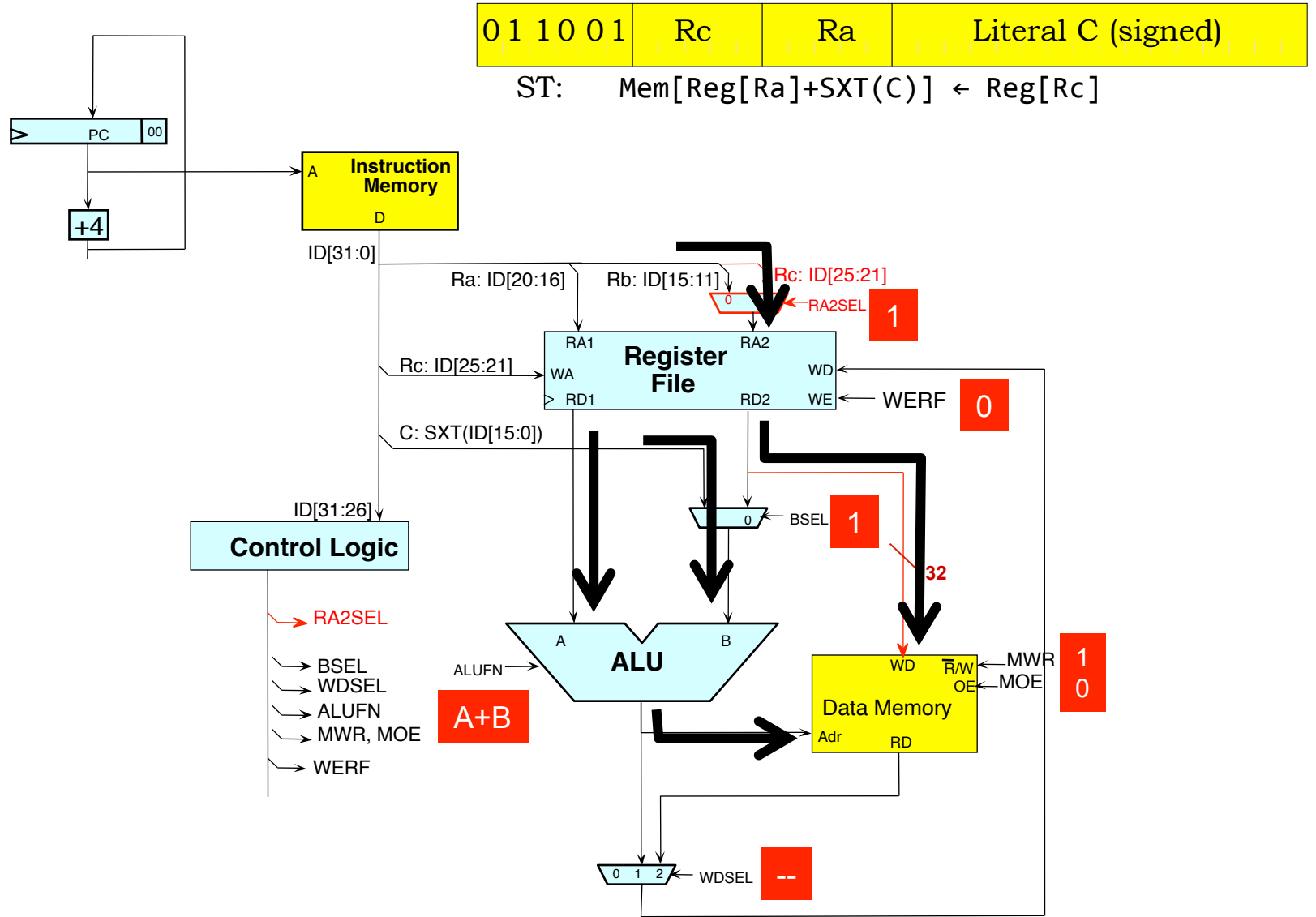


# JMP Instruction

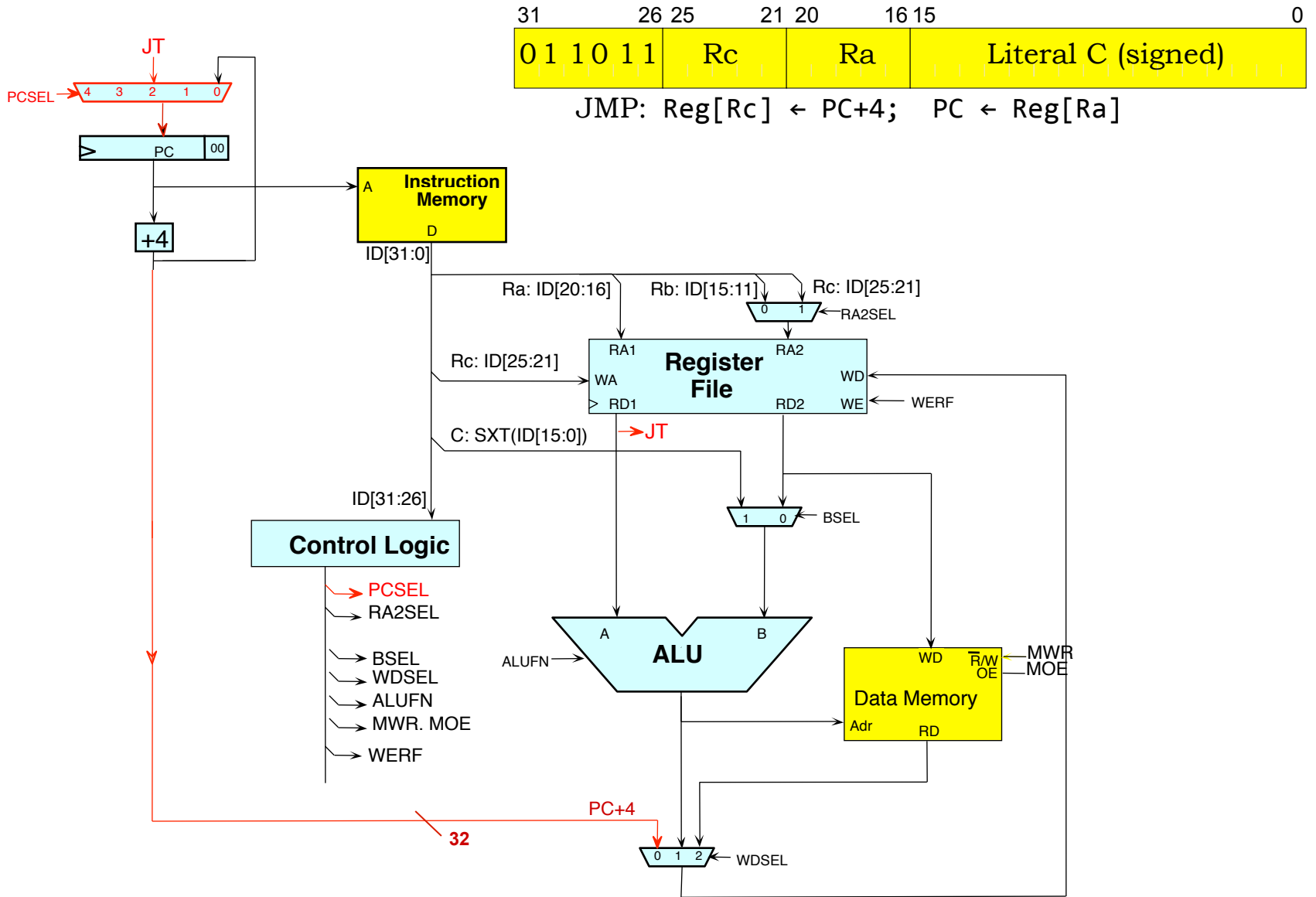

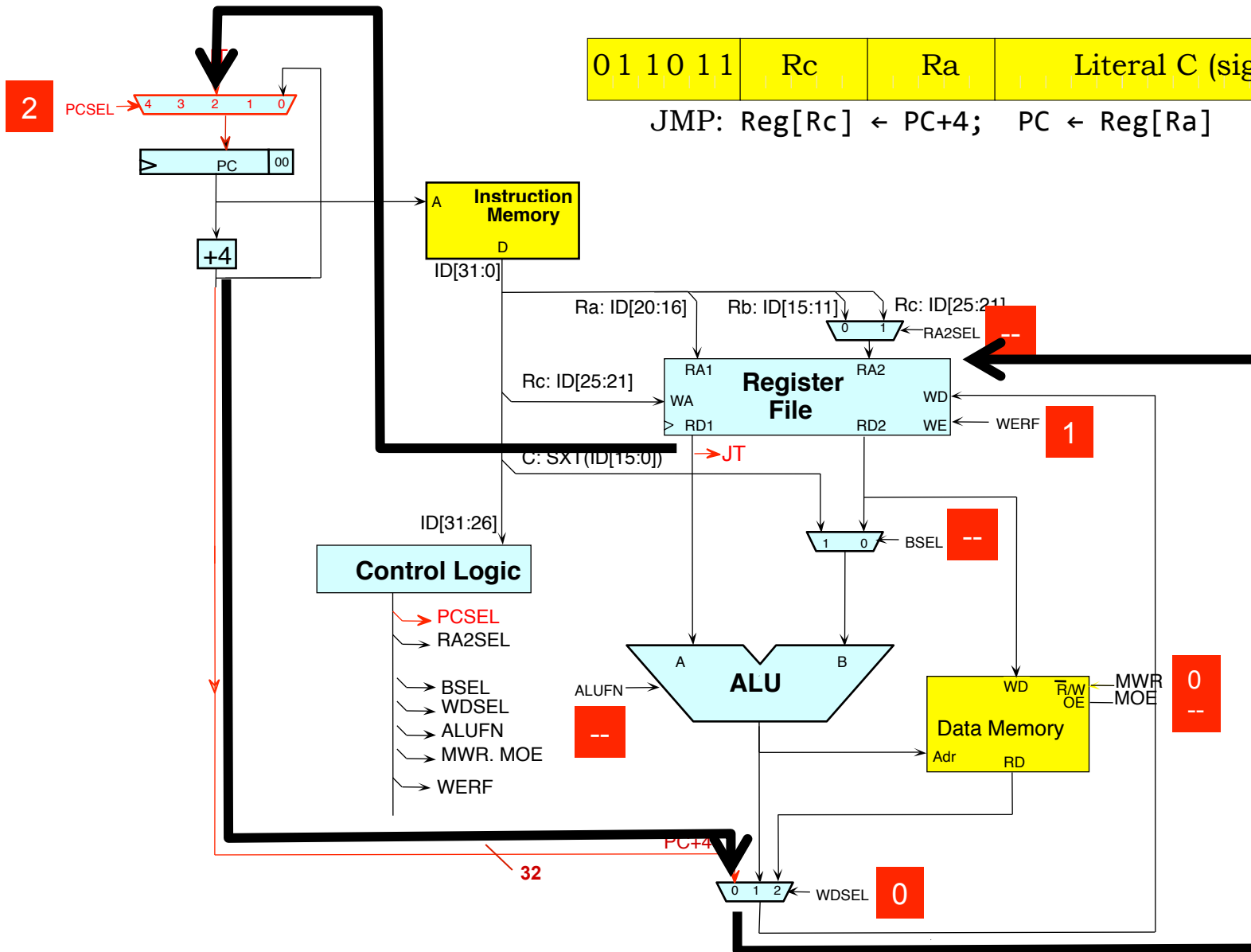
# JMP Instruction



JMP:  $\text{Reg}[Rc] \leftarrow \text{PC}+4$ ;  $\text{PC} \leftarrow \text{Reg}[Ra]$




# BEQ/BNE Instructions

 


BEQ:  $\text{Reg}[Rc] \leftarrow \text{PC}+4$ ; if  $\text{Reg}[Ra]=0$  then  $\text{PC} \leftarrow (\text{PC}+4)+4*\text{SXT}(C)$



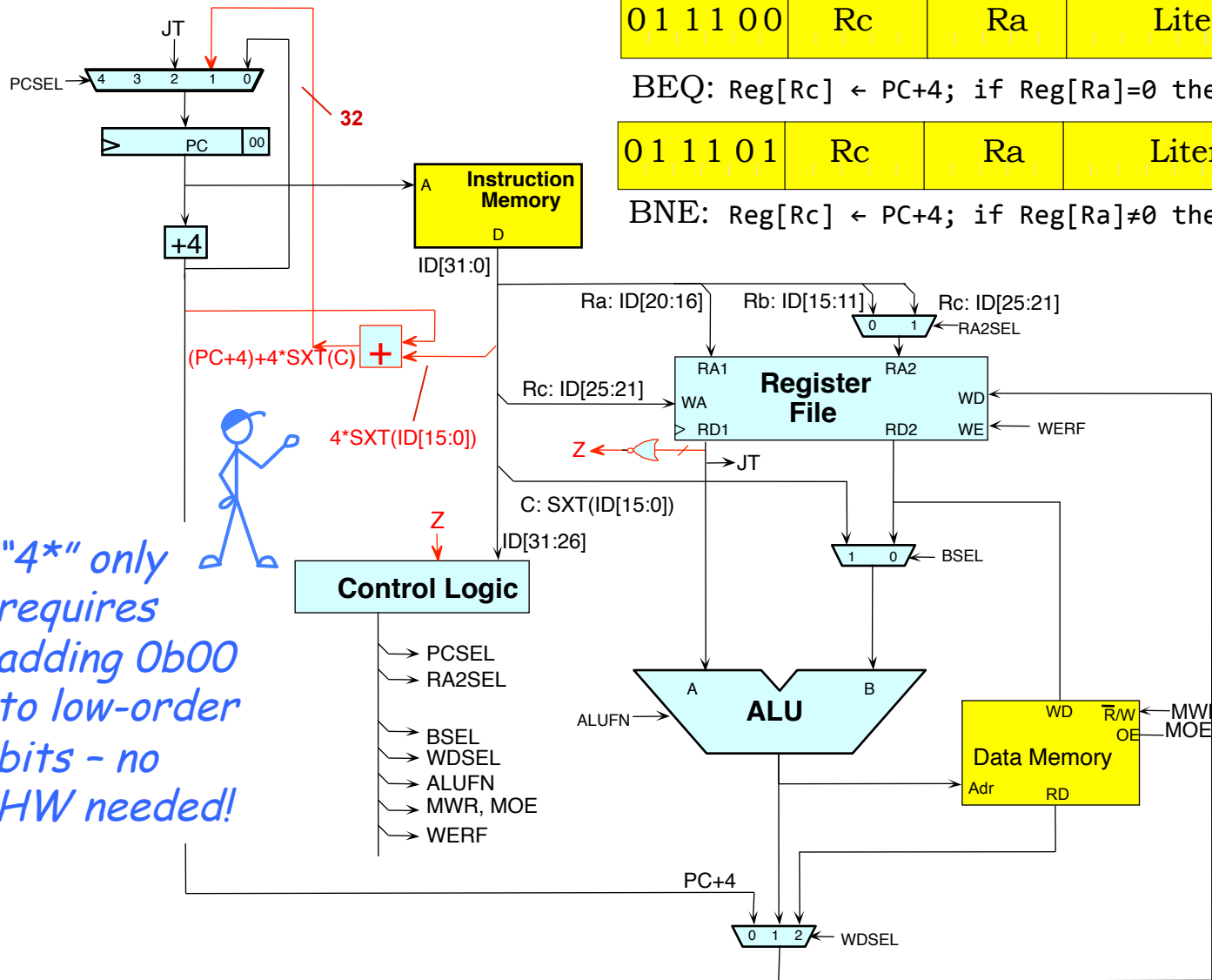BNE:  $\text{Reg}[Rc] \leftarrow \text{PC}+4$ ; if  $\text{Reg}[Ra]\neq 0$  then  $\text{PC} \leftarrow (\text{PC}+4)+4*\text{SXT}(C)$



# BEQ/BNE Instructions

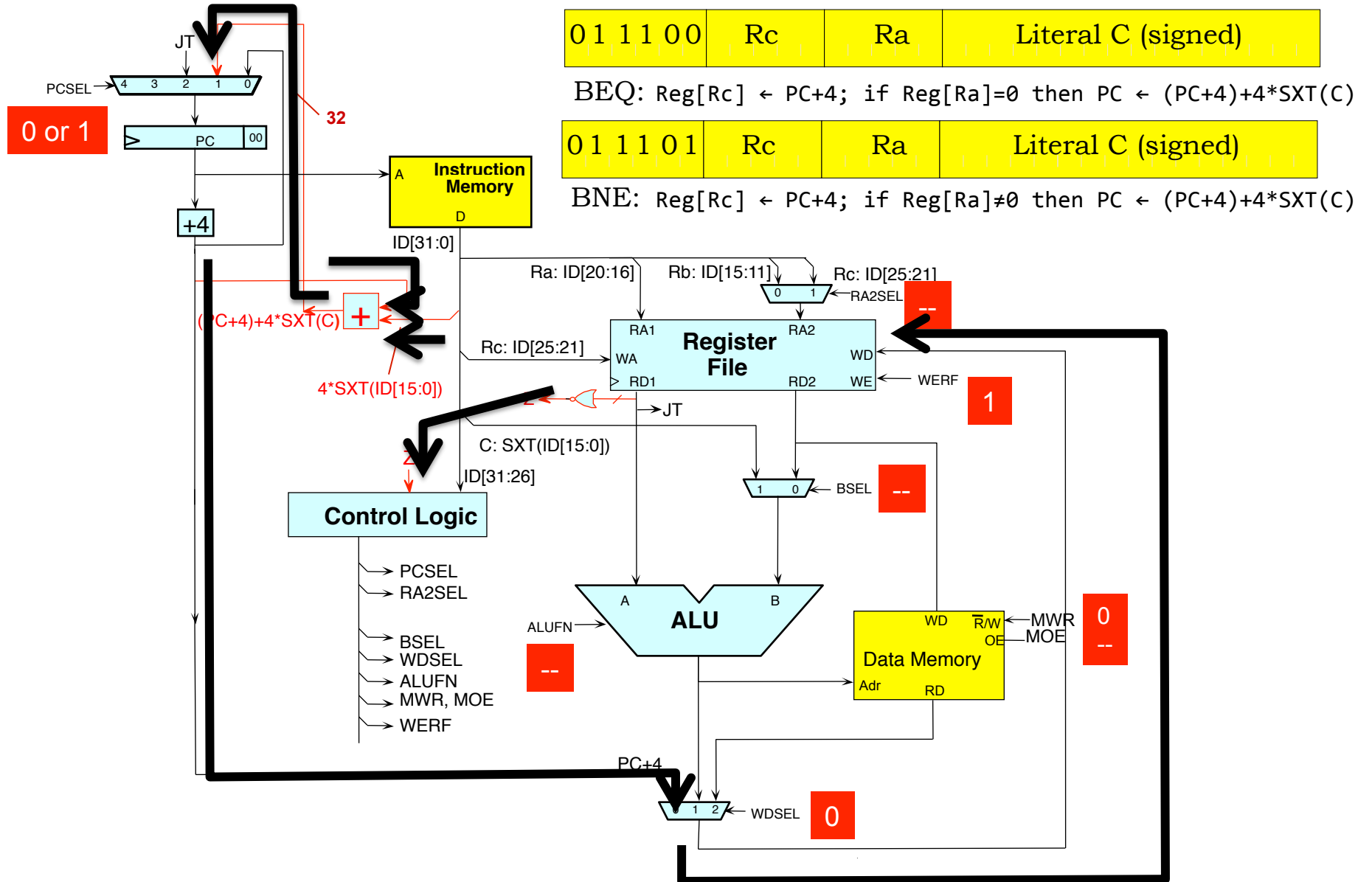

0 1 1 1 0 0    Rc    Ra    Literal C (signed)

BEQ:  $\text{Reg}[Rc] \leftarrow \text{PC}+4$ ; if  $\text{Reg}[Ra]=0$  then  $\text{PC} \leftarrow (\text{PC}+4)+4*\text{SXT}(C)$

0 1 1 1 0 1    Rc    Ra    Literal C (signed)

BNE:  $\text{Reg}[Rc] \leftarrow \text{PC}+4$ ; if  $\text{Reg}[Ra]\neq 0$  then  $\text{PC} \leftarrow (\text{PC}+4)+4*\text{SXT}(C)$

# Load Relative Instruction



LDR:  $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SXT}(C)]$

What's Load Relative good for anyway??? I thought

- Code is “PURE”, i.e. READ-ONLY; and stored in a “PROGRAM” region of memory;
- Data is READ-WRITE, and stored either
  - On the STACK (local); or
  - In some GLOBAL VARIABLE region; or
  - In a global storage HEAP.

So why have an instruction designed to load data that's “near” the instruction???

Addresses & other large constants

```
C: X = X * 123456;
```


BETA:

```
LD(X, r0)
LDR(c1, r1)
MUL(r0, r1, r0)
ST(r0, X)
```


...

```
c1: LONG(123456)
```

# LDR Instruction

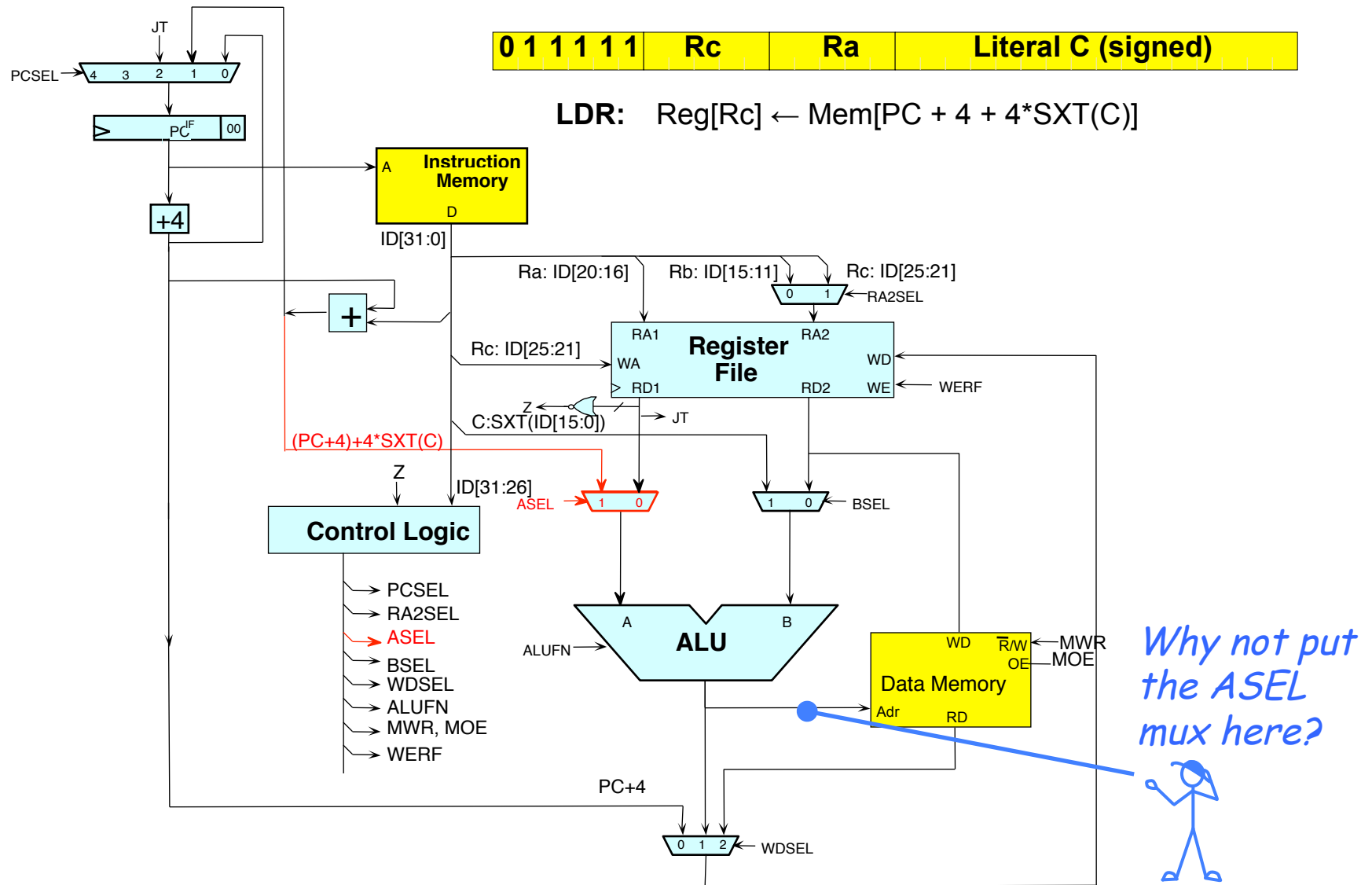

# LDR Instruction

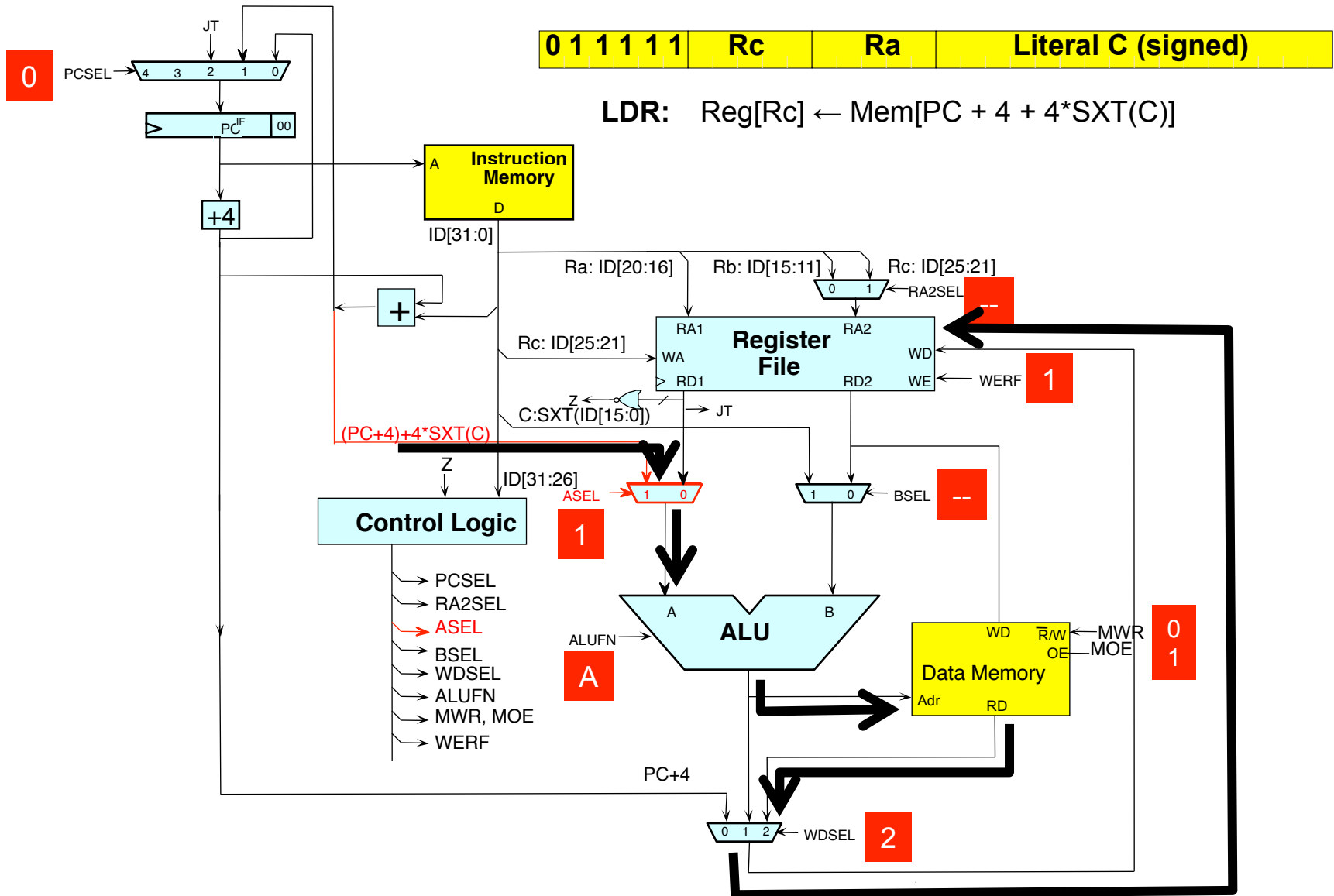



# Exceptions


- What if something bad happens?
  - Execution of an illegal opcode
  - Reference to non-existent memory
  - Divide by zero
- Or maybe just something unanticipated
  - User hits a key
  - A packet comes in via the network
- Exceptions let us handle these cases in software:
  - Treat each case as an (implicit) procedure call
  - Procedure handles problem, returns to interrupted program
  - Transparent to interrupted program!
  - Important added capability: handlers for certain errors (illegal opcodes), can extend ISA using software

# Exception Processing


- Plan:
  - Interrupt running program
  - Invoke exception handler (like a procedure call)
  - Return to continue execution
- Exception and interrupt terms often used interchangeably, with minor distinctions:
  - **Exceptions** usually refer to **synchronous events**, generated by program (e.g., illegal instruction, divide-by-0, illegal address)
  - **Interrupts** usually refer to **asynchronous events**, generated by I/O devices (e.g., keystroke, packet received, disk transfer complete)
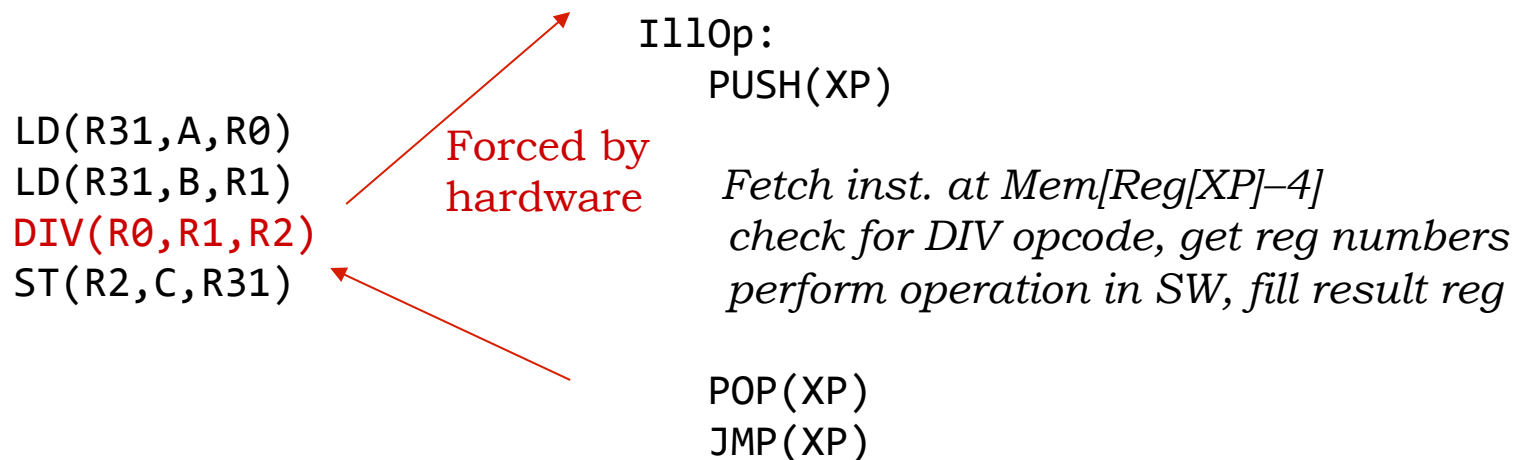
# Exception Implementation

- Instead of executing instruction, fake a procedure call
  - Save current PC+4 (as branches do)
  - Load PC with exception vector: 0x4 for synchronous events, 0x8 for asynchronous events
- We save PC+4 in register R30 (which we call XP)
  - ... and prohibit programs from using XP (why?)
- Example: DIV unimplemented




# Exceptions

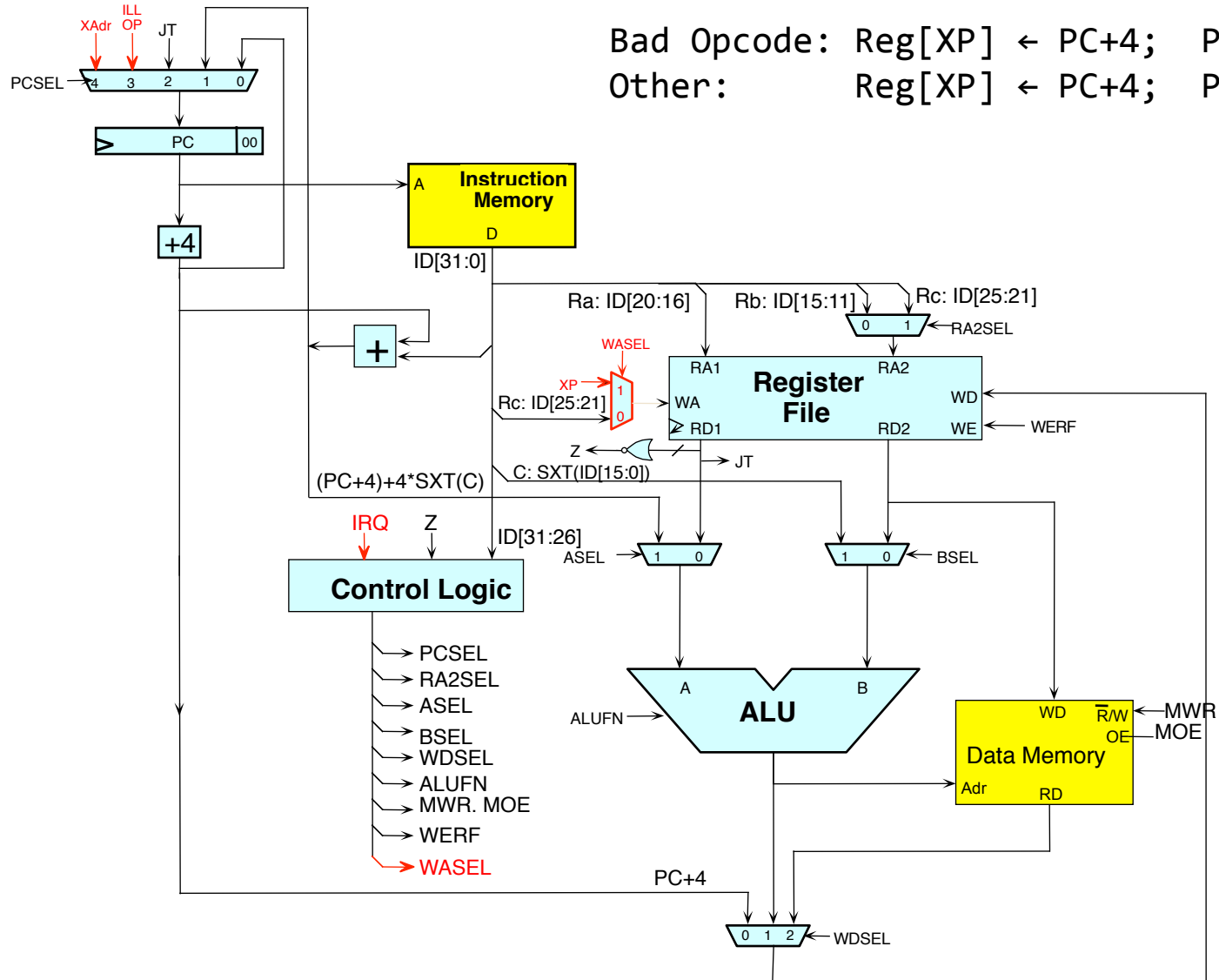


Bad Opcode:  $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$ ;  $\text{PC} \leftarrow \text{"I11Op"}$   
 Other:  $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$ ;  $\text{PC} \leftarrow \text{"Xadr"}$
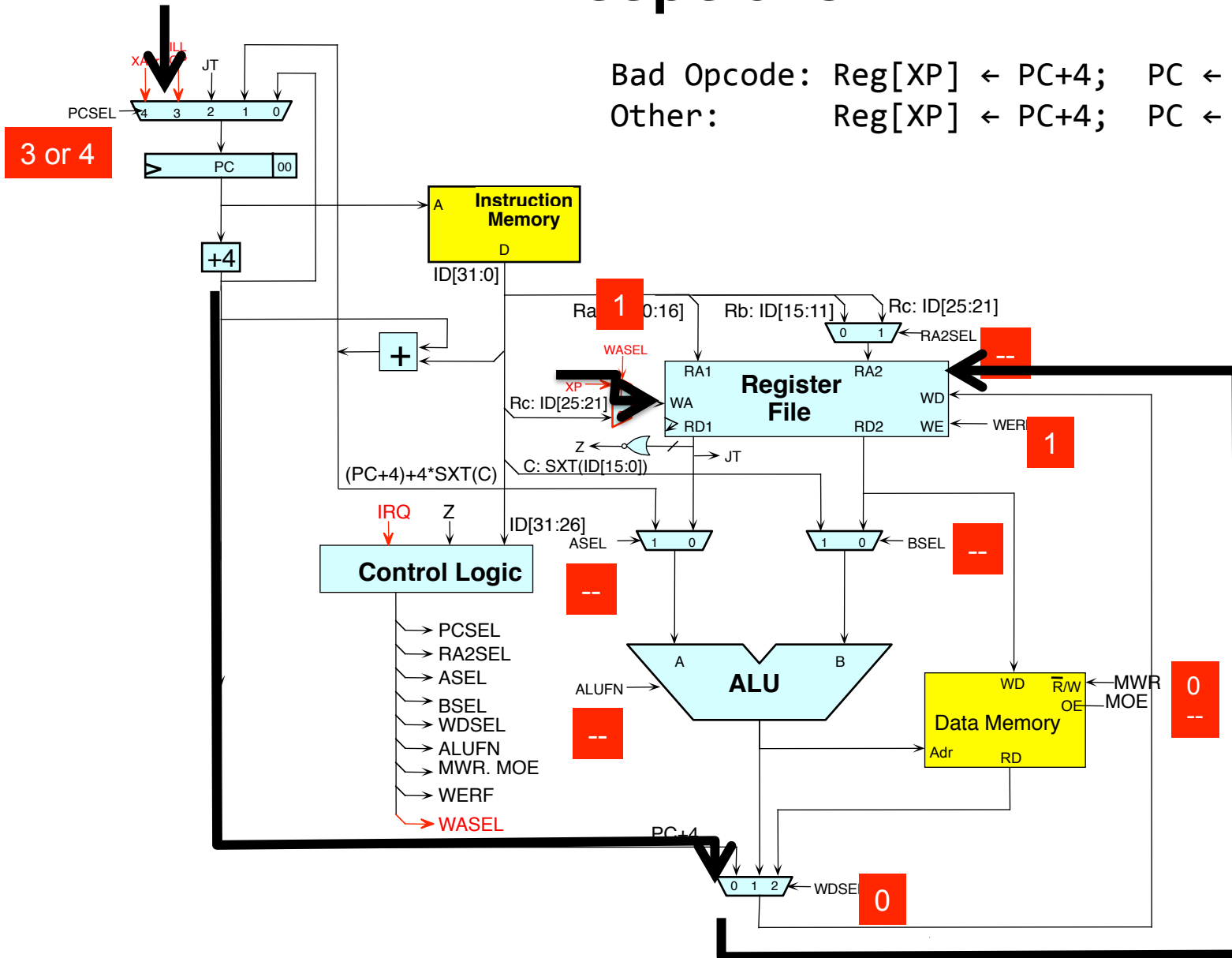
# Exceptions

Bad Opcode:  $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$ ;  $\text{PC} \leftarrow \text{"I110p"}$   
 Other:  $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$ ;  $\text{PC} \leftarrow \text{"Xadr"}$



# Beta: Our “Final Answer”

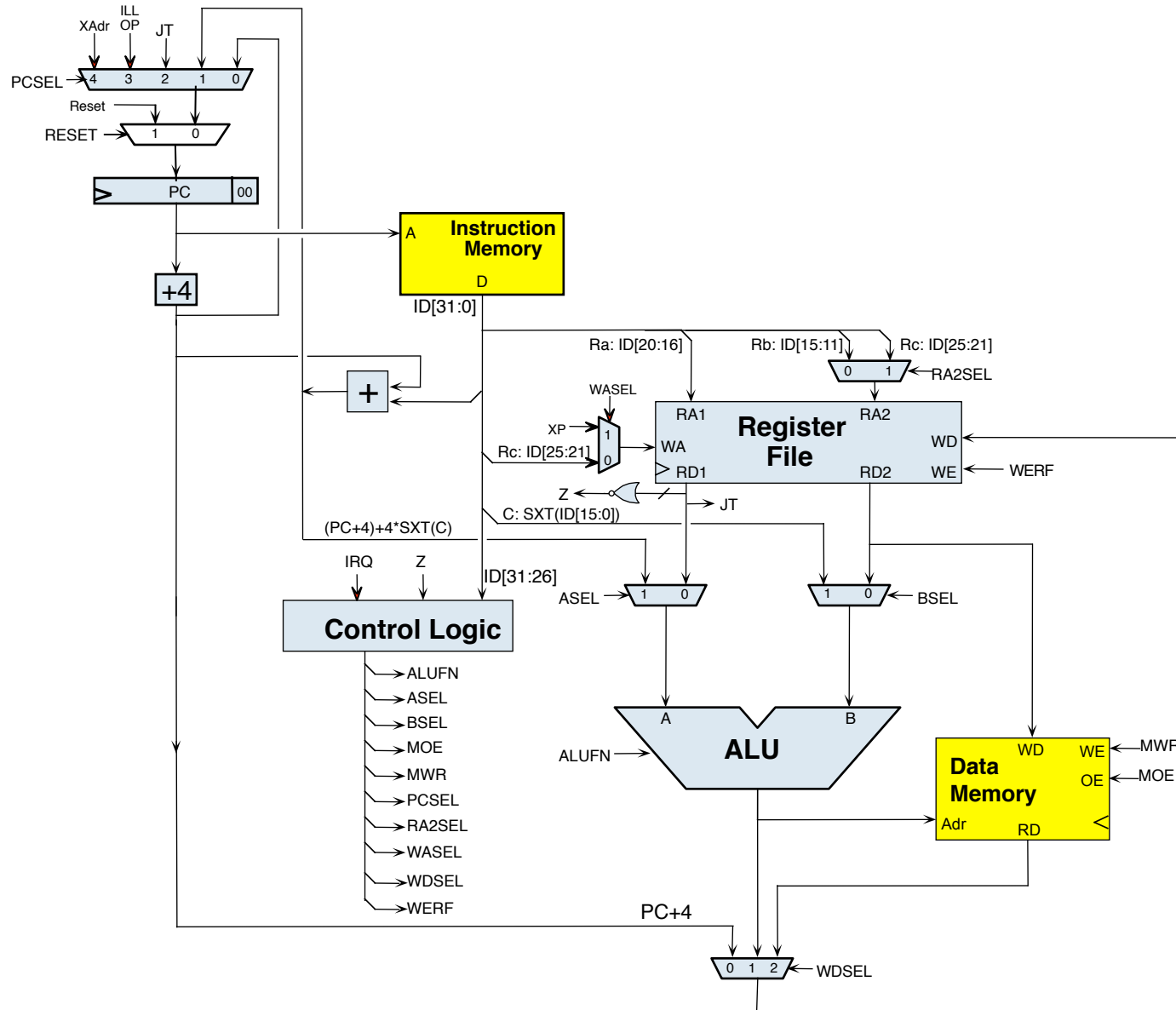


# Control Logic

	RESET	IRQ	OP	OPC	LD	LDR	ST	JMP	BEQ	BNE	ILLOP
ALUFN	--	--	F(op)	F(op)	"+"	"A"	"+"	--	--	--	--
ASEL	--	--	0	0	0	1	0	--	--	--	--
BSEL	--	--	0	1	1	--	1	--	--	--	--
MOE	--	--	--	--	1	1	0	--	--	--	--
MWR	0	0	0	0	0	0	1	0	0	0	0
PCSEL	--	4	0	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	3
RA2SEL	--	--	0	--	--	--	1	--	--	--	--
WASEL	--	1	0	0	0	0	--	0	0	0	1
WDSEL	--	0	1	1	2	2	--	0	0	0	0
WERF	--	1	1	1	1	1	0	1	1	1	1
 
## Implementation choices:

- 64-location ROM indexed by opcode with external logic to handle changes due to Z and IRQ inputs
- Entirely combinational logic (faster, but much more work!)

*Is **that** all there is to building a processor???*



*No. You've gotta print up all those little "Beta Inside" stickers.*

